

Addressing the Challenges of Reset Verification in SoC Designs

Chris Kwok

Priya Viswanathan

Ping Yeung



The Reset Problem

- There are many types of resets:
 - Power-on resets, software resets, hardware resets, debug reset, etc.
- Errors in reset can lead to metastability, glitches, corrupt simulation with X or even failure to power on

Current Methods

- Simulation, simulation, simulation
- Issues usually found at late-stage, after long gate-level simulation

Purpose



- Bring awareness of the reset problem
- What kind of reset problems exist
- What kind of solutions available

Common Problems

- Reset Distribution Tree
 - Reset tree construction issues
- Reset Usage
 - Issues with how reset is used

Reset Tree Problem

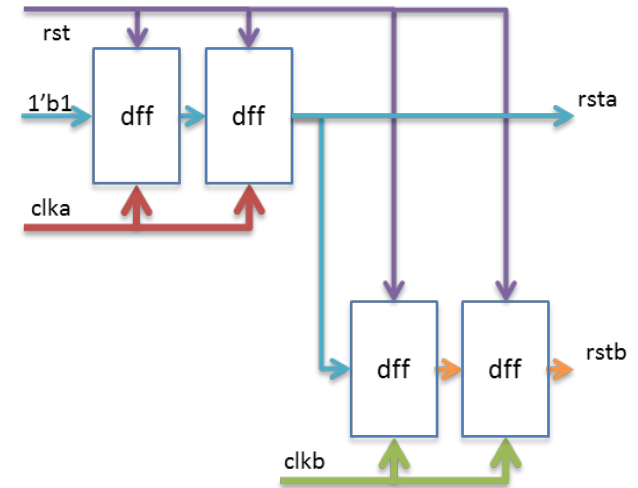 - Mixed asynchronous/synchronous types
- Overlapping set and reset
- Reset crossing clock domains



Reset with mixed types

- Signal 'rst_n' is used as asynchronous to 'q1' and synchronous to 'q2'
- Usually indicates a misunderstanding of the reset

```
always @(posedge clk or negedge rst_n)
  if (!rst_n)
    q1 <= 1'b0;
  else
    q1 <= d;


always @(posedge clk)
  if (!rst_n)
    q2 <= 1'b0;
  else
    q2 <= d;
```

Overlapping set and reset

- Register has both asynchronous set and reset signals
- If both set & reset are active, lead to mismatch between simulation & synthesis
- Some technology libraries do not have register with both asynchronous set & reset

```
always @(posedge clk or negedge rst_n or negedge set_n)
  if (!rst_n)
    q1 <= 1'b0;
  else if (!set_n)
    q1 <= 1'b1;
  else
    q1 <= d;
```


Reset crossing clock domains

 


- The reset tree spans multiple clock domains
- Reset signals need to be **synchronized** to the target clock domain before used.

Reset Synchronizer

- Why do we need reset synchronizer?
- How is reset synchronizer used?
- What other problems related to reset synchronizer?



Asynchronous Reset

 - Asynchronous reset signal can change anytime
- If reset 'RST' is de-asserted close to the clock edge
 - Violates the recovery time
 - Leads to metastability




How to fix it?

  - Synchronize before use
 - Typical synchronizer is 2 back-to-back flops
- Ensure asynchronous assertion and synchronous de-assertion
- X will not be seen at the output of the synchronizer




Reset Synchronizer used wrong polarity

 - Register reset by the synchronizer is using active high reset, while the synchronizer is an active-low reset.



Reset Synchronizer used with wrong clock

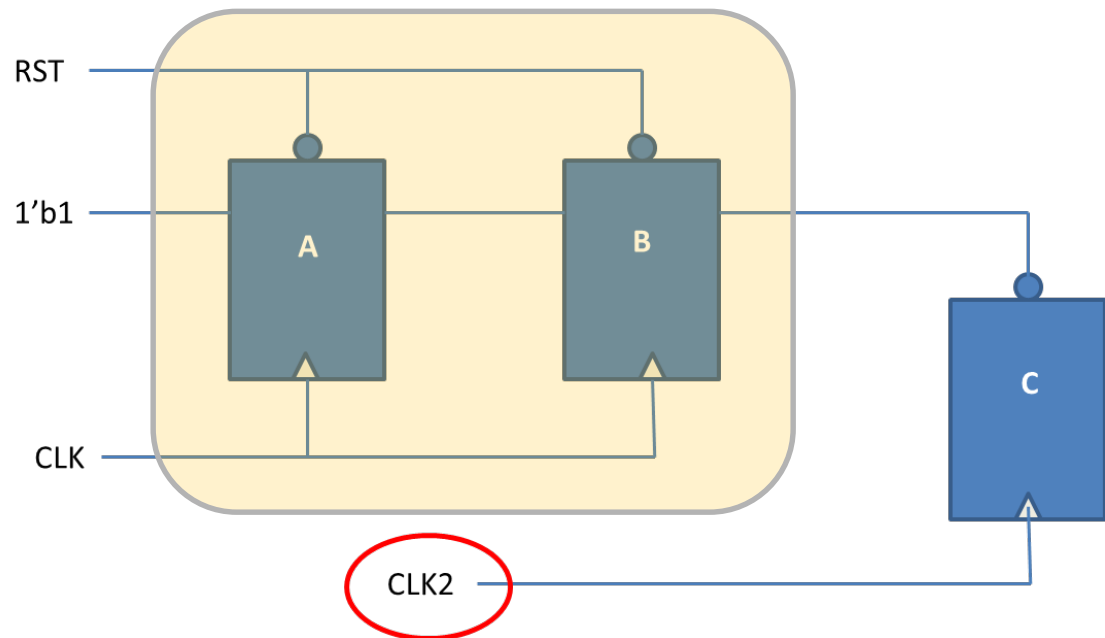- Downstream register using reset synchronizer is clocked in a different clock (CLK2) from reset synchronizer (CLK)
- Caught by CDC tool




Reset Domain Crossing

- What is reset domain?
- What is reset domain crossing (RDC) ?



What is a Reset Domain?

 - What constitute a reset domain?
 - Type: Synchronous / Asynchronous
 - Polarity : Active-high / Active-low
 - Value : 1 (set) / 0 (reset)
- Registers reset by reset of the same attributes are considered to be in the same reset domain




What is Reset Domain Crossing (RDC)?

 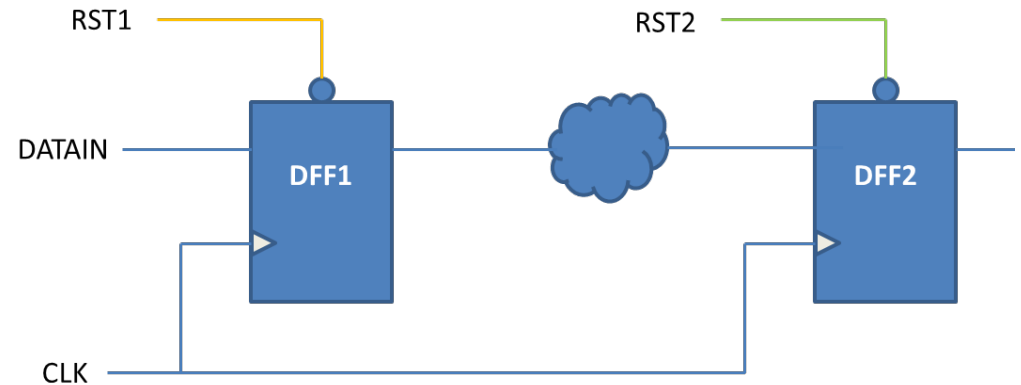- If RST1 is asserted while RST2 is not asserted, DFF2 can sample corrupted data.



RDC – Incorrect Delay Sequences

 

- Assertion of RST will prematurely cause DFF2 to reset while DFF2 is still in functional state.
 - Causes incorrect data at the downstream logic
- If RST is only asserted 2 cycles, then when RST deasserts, DFF2 will be corrupted by DFF1 before DFF1 gets the reset signal.

Proposed Verification Solution

- Static Analysis
 - Automatically analyzes the design and report obvious errors
- Simulation with X-propagation
 - Propagate X values to cause testbench failure
- Formal Verification
 - Exhaustive Analysis on special properties

Design Blocks

Design Complexity	Block 1	Block 2	Block 3
Number of registers	305	47016	43622
Number of latches	0	592	0
Number of RAMs	2	0	64
Number of Gate-level modules	0	88	20

Reset/Clock domains information	Block 1	Block 2	Block 3
Number of reset domains	3	36	48
Number of clock domains	9	5	12
Number of clocks crossing reset domains	2	3	6
Number of resets crossing clock domains	2	5	5

- Verilog RTL design blocks
- FIFO Controller, Functional Controller, Networking Unit

Reset/Clock Relationship

- Questa Reset Check was used

Reset Groups


Name	ldtRxWinkClk	txcRx2p	ldtTxWinkClk	h_extsrcKin	h_extxcKin	h_mdC	_or_200	_pcb
..._inloop_inlp_rxenable			R: 3, L: 0					
...loop_rst_inlp_rxenable	R: 1, L: 0							
...mux.htext_ldtRxSync				R: 1, L: 0				
...ht.ht_mux.rxsync_det				R: 6, L: 0				
...SYNC_ACTL_0.reset_N							R: 23, L: 0	
...RxWinkRstPreAsync_N	R: 644, L: 0							
...0.ldtRxWinkSyncSized	R: 7, L: 0						R: 17, L: 0	
...SIZER_0.resetAsync_N	R: 151, L: 0							
...TXSYNC_RESET_0.rst			R: 87, L: 0					
...ch.UDP_U_OFFR_51.q	R: 3, L: 0							
..._RESET.ldtRxSyncArm								

Static Analysis Results

Results of static analysis	Block 1	Block 2	Block 3
Missing asynchronous reset synchronizer		√	
Unexpected gate in reset tree	√	√	
Reset signal used as asynchronous and synchronous			√
Good asynchronous reset synchronizer		√	

Number of RDCs	Block 1	Block 2	Block 3
Across same clock domain	3	25966	225
Across different clock domains	0	2618	42


Sample RDC Violation

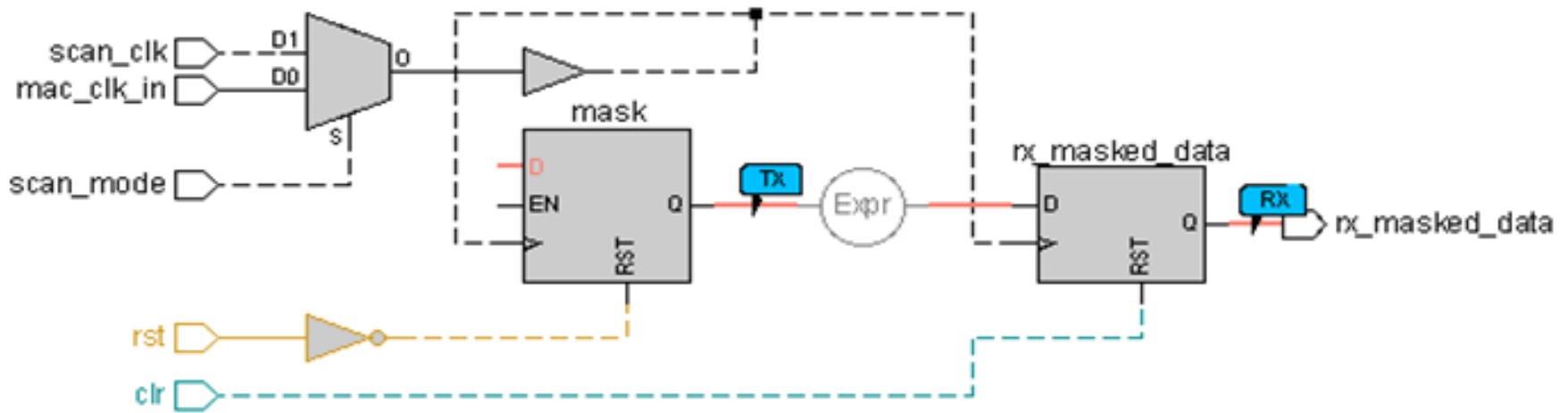


- Signals “mask” and “rx_masked_data” are in the same clock domain
- “rst” and “clr” are of different reset domain

Formal Results

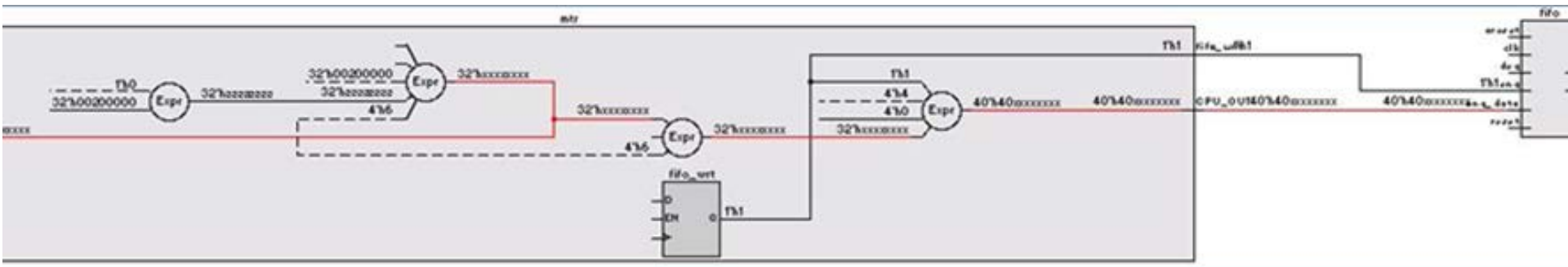- To validate a FIFO is functioning properly
- Questa Formal was used



Formal Results

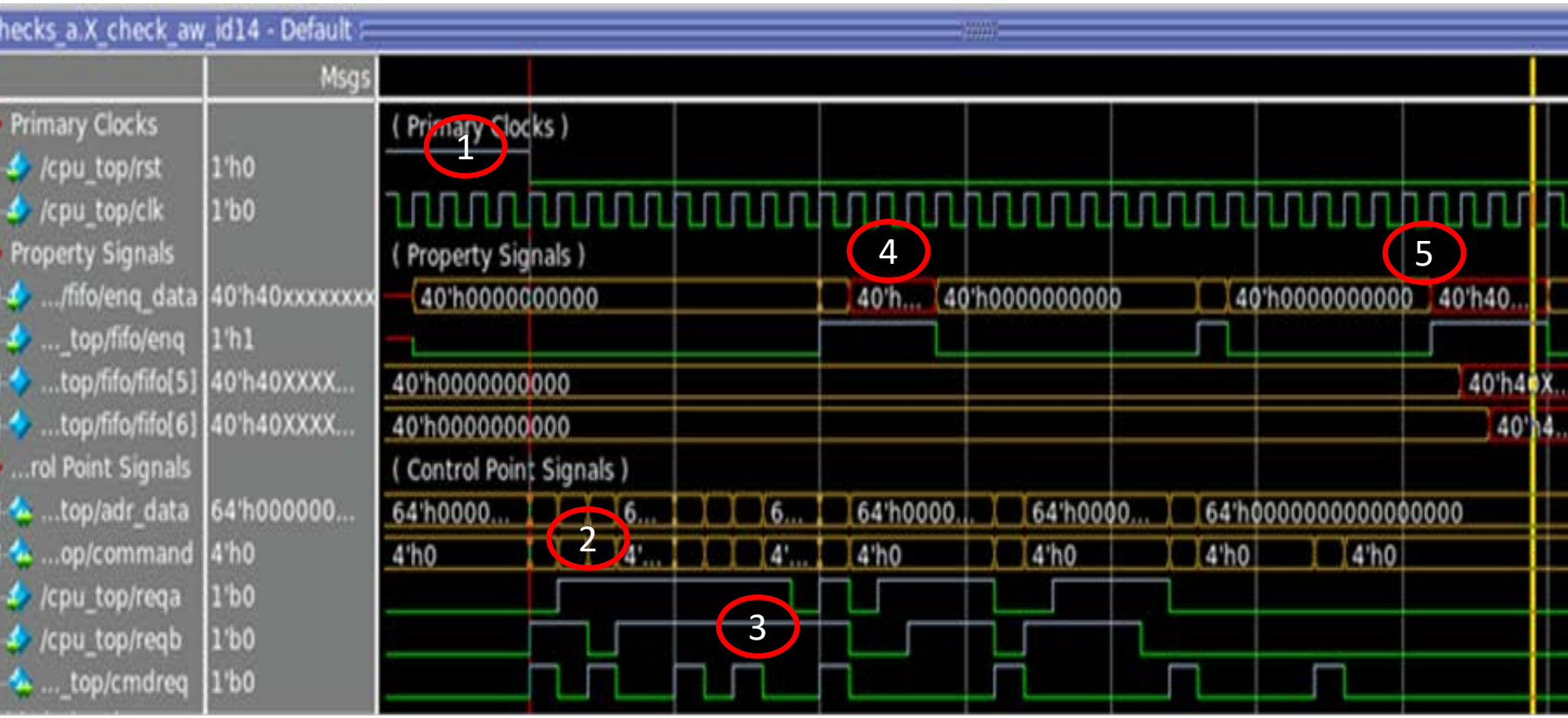

Summary

- As SoC designs get complex, reset problems become harder to catch
 - Traditional solution no longer sufficient
- We discussed:
 - Several common reset problems presented
 - Proposed solution discussed
 - Using the method, results were presented