

Full Flow Clock Domain Crossing - From Source To Sí


Mark Litterick, Verilab, Germany




Introduction

- Overview
 - pre-silicon flow, metastability & MTBF, timing analysis for CDC & synchronizers
- Physical Requirements
 - 2FF, parallel, handshake & phase-detect synchronizers
 - timing requirements & failure modes
- Continuity & Closure
 - pragmatic solutions for encapsulation
 - SVA timing checks for continuity
 - closure using gate-level CDC analysis, constraints management & CDC review

Pre-Silicon Flow

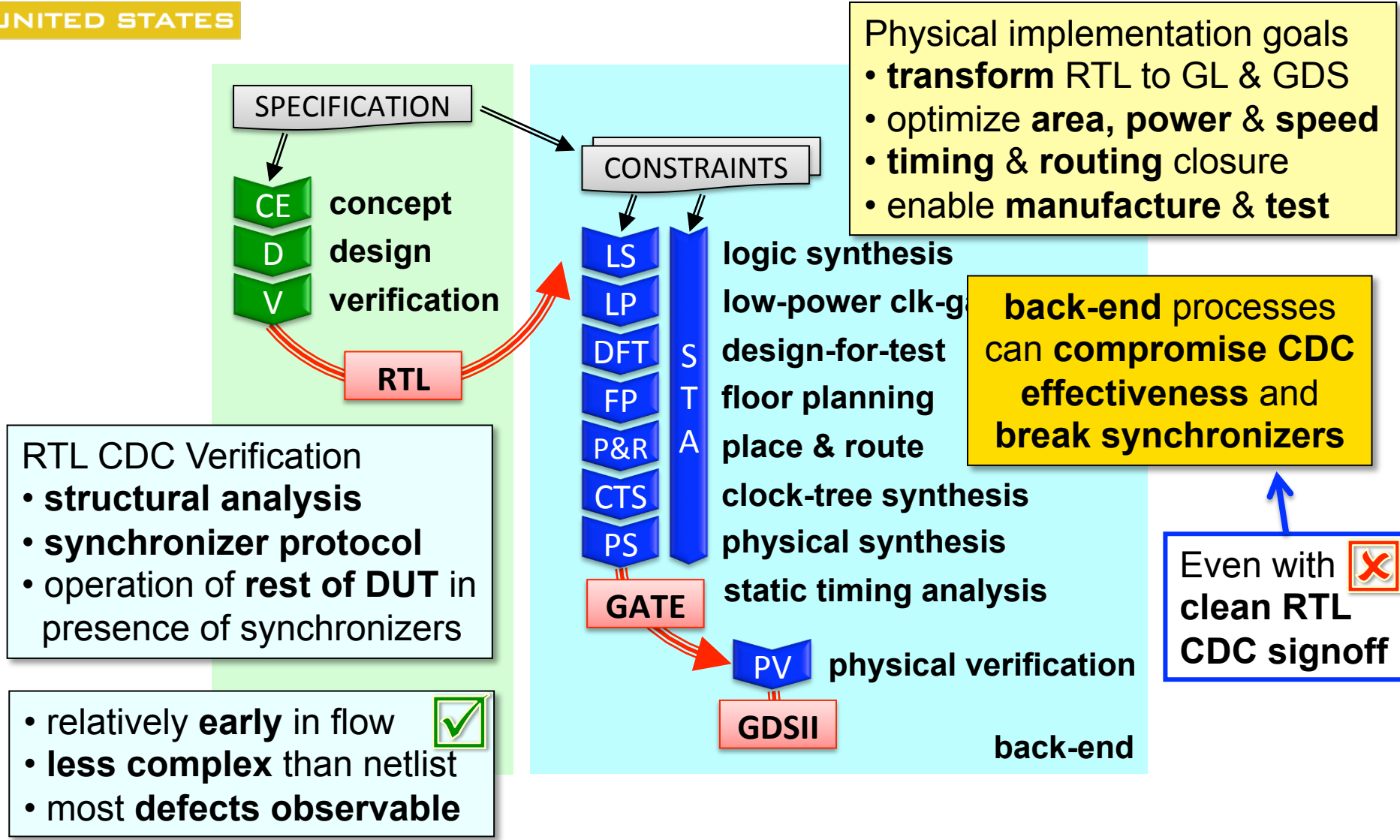

Metastability & MTBF

 

$$MTBF = \frac{e^{T_s/T_c}}{T_w F_c F_d}$$

Technology & Implementation

T_s = settling window

T_c = settling time constant

T_w = window of susceptibility


F_c = clock frequency

F_d = data update rate

Concept & Application

- **Violation of setup or hold times causes metastability**
 - **unstable** state eventually decays to 0 or 1, but **unpredictable!**
 - **real-life** transistor effect, not observable in simulations or formal
 - **cannot be avoided**, must be designed around & managed
- **Mean Time Between Failures (MTBF)**
 - **probability** of metastability **not decaying** to stable legal value in time for the next sampling event => catastrophic failure


Timing Arcs & CDC Paths

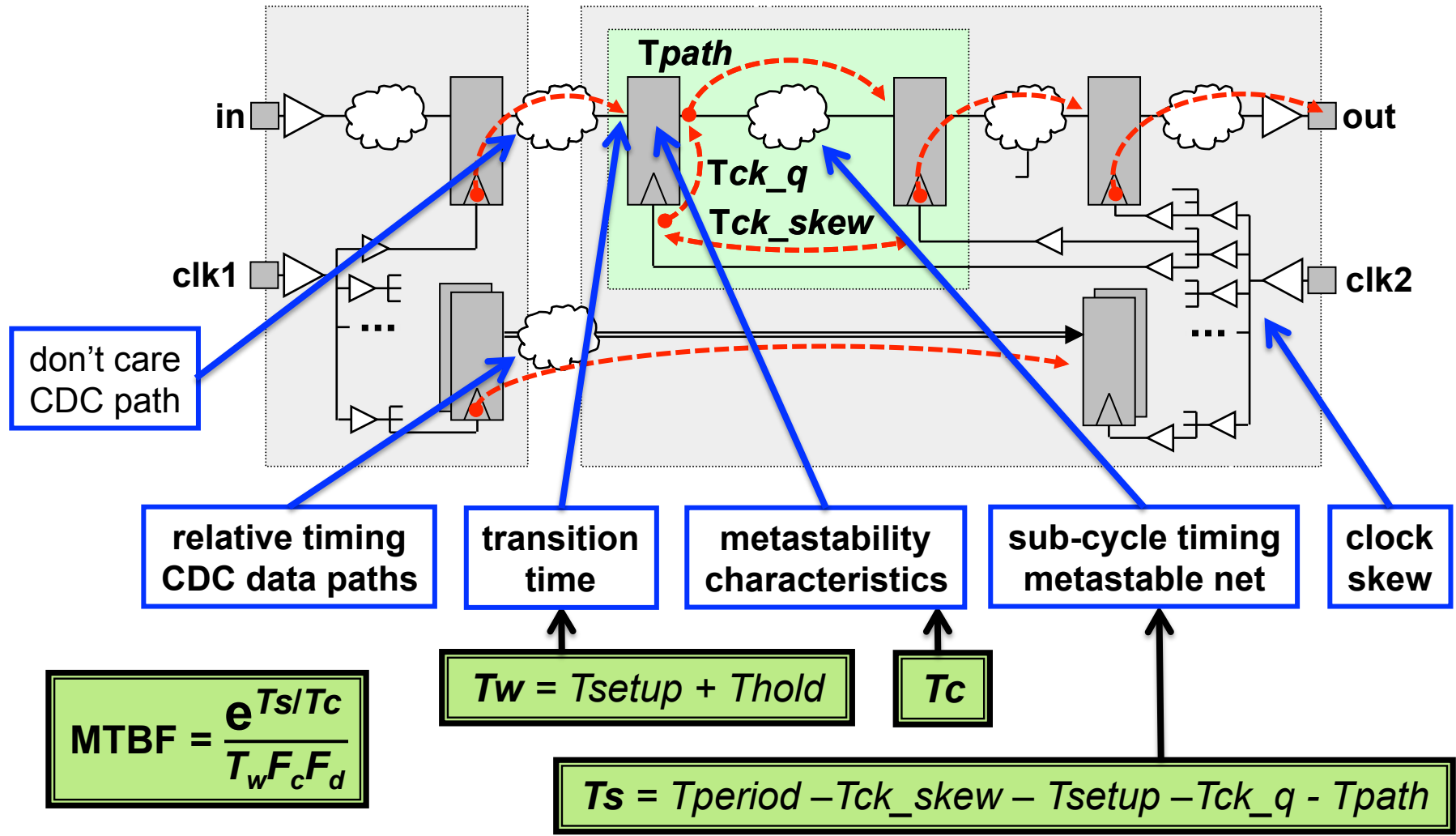

2FF Synchronizer

RTL CDC Requirements

 - no logic on CDC path
- no glitches on D input
- D stability > 2 clock f




PHY CDC Requirements

- sub-cycle timing on m
- fast transition time at d_in
- fast metastability damping
- no scan insertion 2nd FF
- tight clock-skew tolerance


glitch =
 unsampled
 narrow pulse
 (\approx many src clks)

RTL
 or GL
 sim

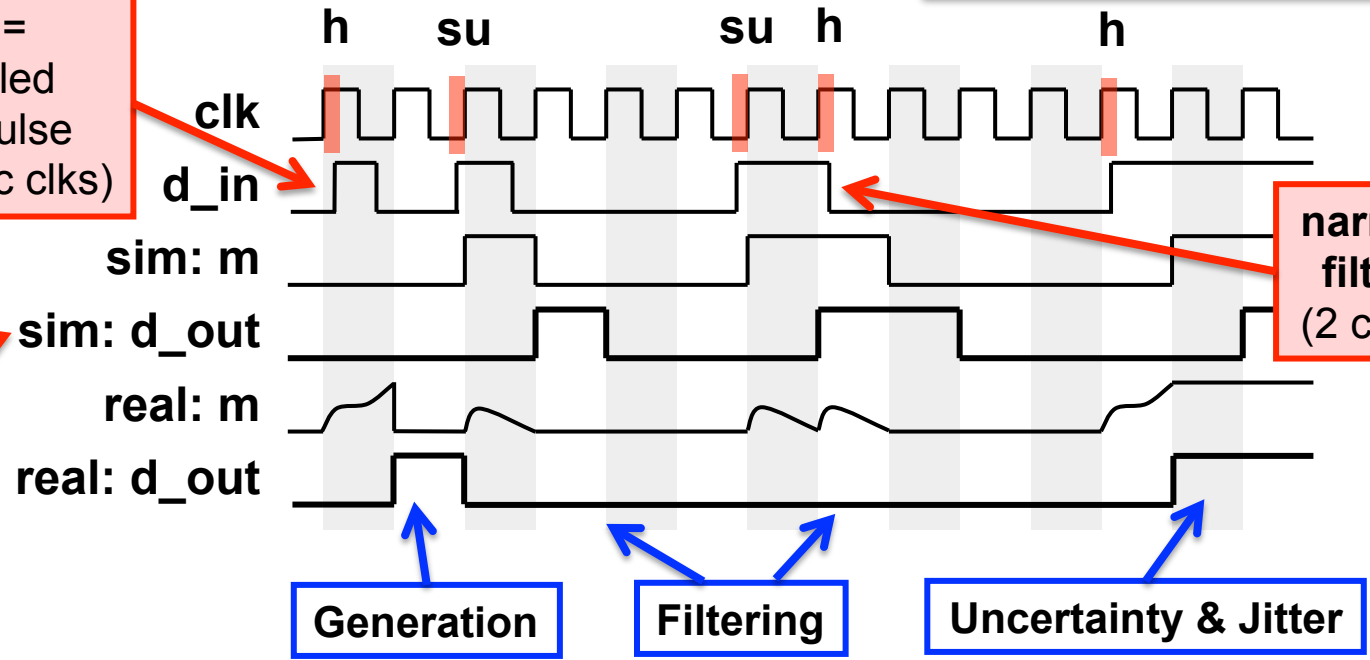

narrow pulse
 filtered out
 (2 clk edges!)

Failure: Sub-Cycle Timing

 

$$MTBF = \frac{e^{Ts/Tc}}{T_w F_c F_d}$$

$$Ts = T_{period} - T_{ck_skew} - T_{setup} - T_{ck_q} - T_{path}$$

Exponential effect on MTBF


Parallel Synchronizer

RTL CDC Requirements


- **bus is gray-coded** at source (only one bit change per clock)

PHY CDC Requirements

 - **relative timing for all bits** must ensure bus is gray-coded **on arrival** at 1st FFs




only 1 bit *can* go metastable per clk

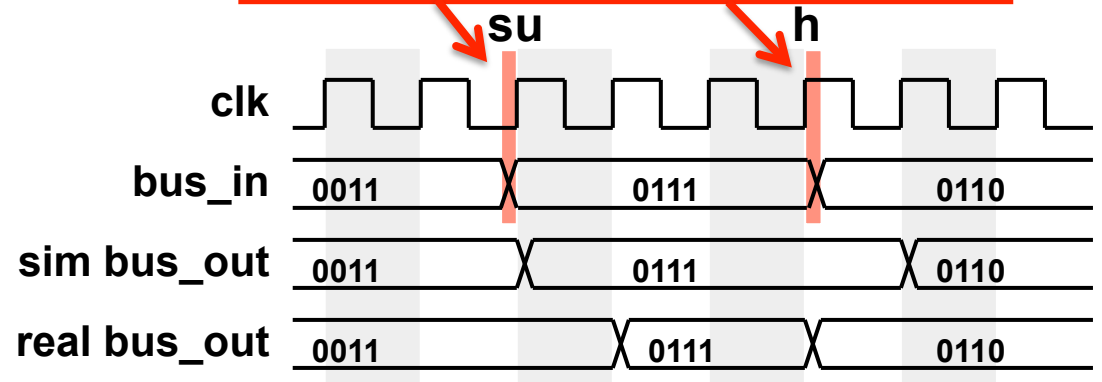

slow-to-fast (all codes transported)

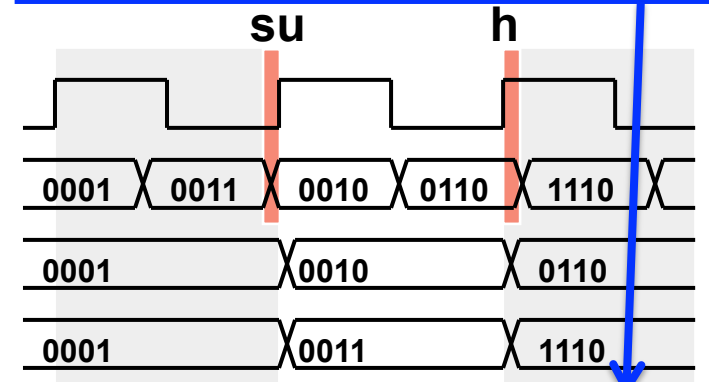no stability check in each 2FF
 no gray-code check @ dest clk



fast-to-slow (some codes dropped)


Failure: Path Variance

CDC bus under-constrained, e.g.

- marked as **false-path** (unconstrained)
- marked as **multi-cycle path** (either clk)
- using slow **destination clock period**
- **default constraints** (slow-speed scan)

No absolute path delay requirement, but **relative timing** for all **parallel paths** must ensure **in-order** and **variance > Tw**

 Pragmatic: **delay** for all **paths** must be **less** than one **source clock period**



Normal failure: **signal reorder** (visible in GLS)

Corner case: **close together** but in-order

Received value **was not sent**

$$[(T_{period_1} + T1) - (T_{ck_skew_1} + T0)] > (T_{setup_2} + Thold_2)$$



Handshake Synchronizer

RTL CDC Requirements

- **full handshake** protocol
- **D stable** until **ack** in **src**

PHY CDC Requirements

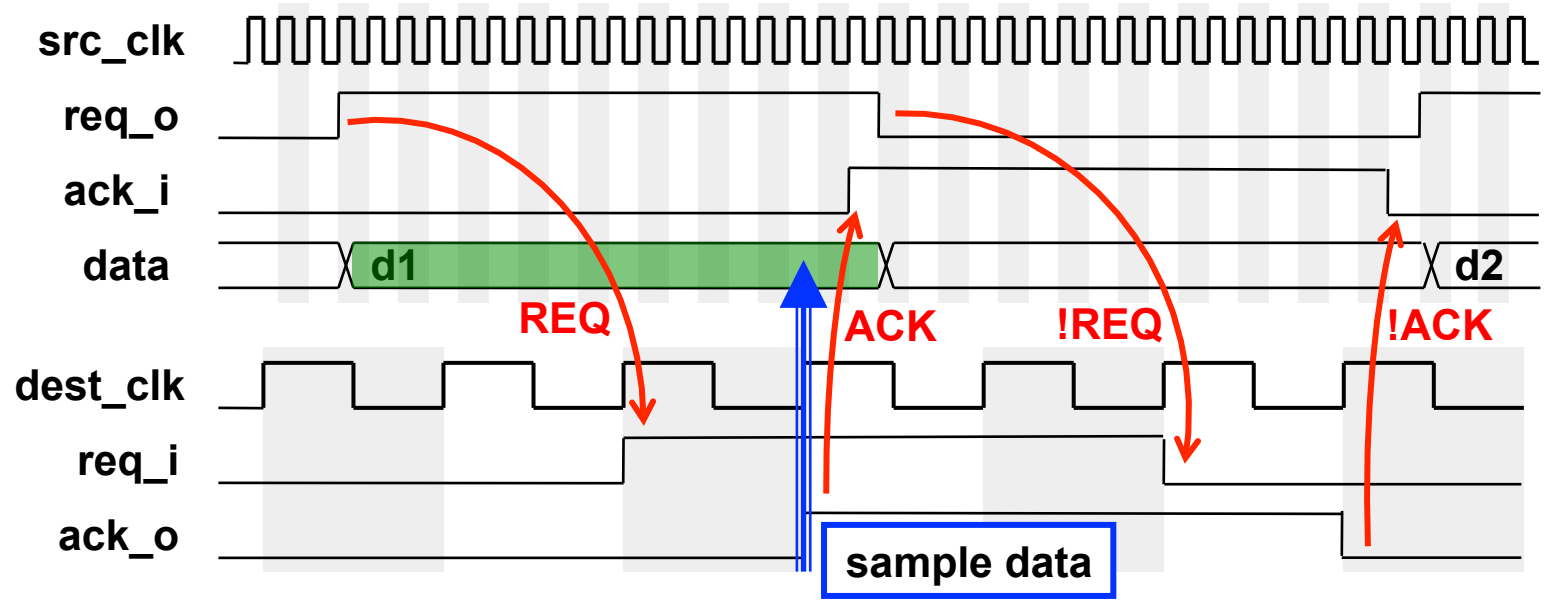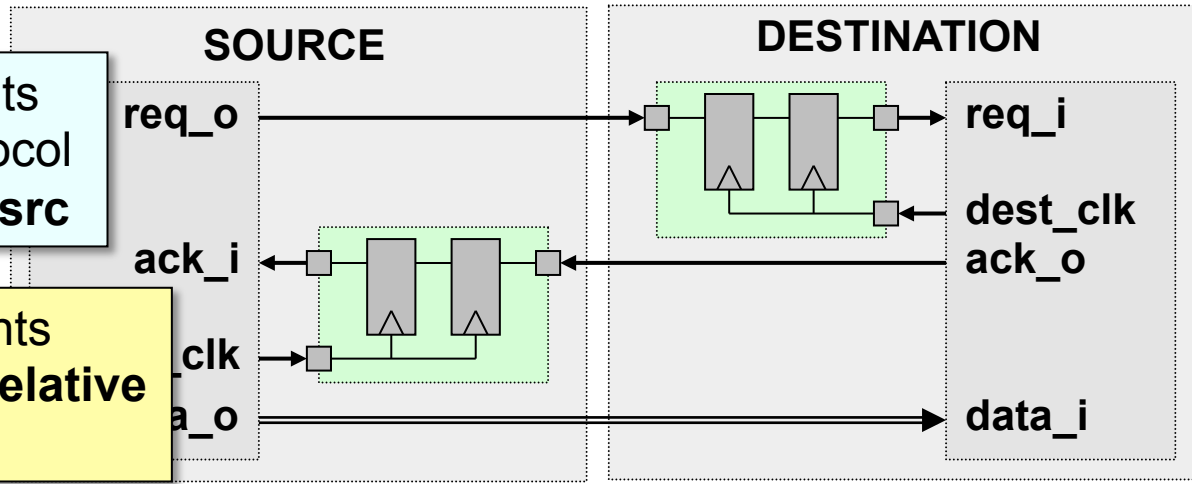- **max delay** on **data** relative to **req** and **dest_clk**




Failure: Slow Path

CDC data under-constrained, e.g.

- marked as **false-path** (unconstrained)
- marked as **multi-cycle path** (src_clk)
- using slow **source clock** period
- **default constraints** (slow-speed scan)


Data has **path delay** requirement, **relative** to req and destination clock

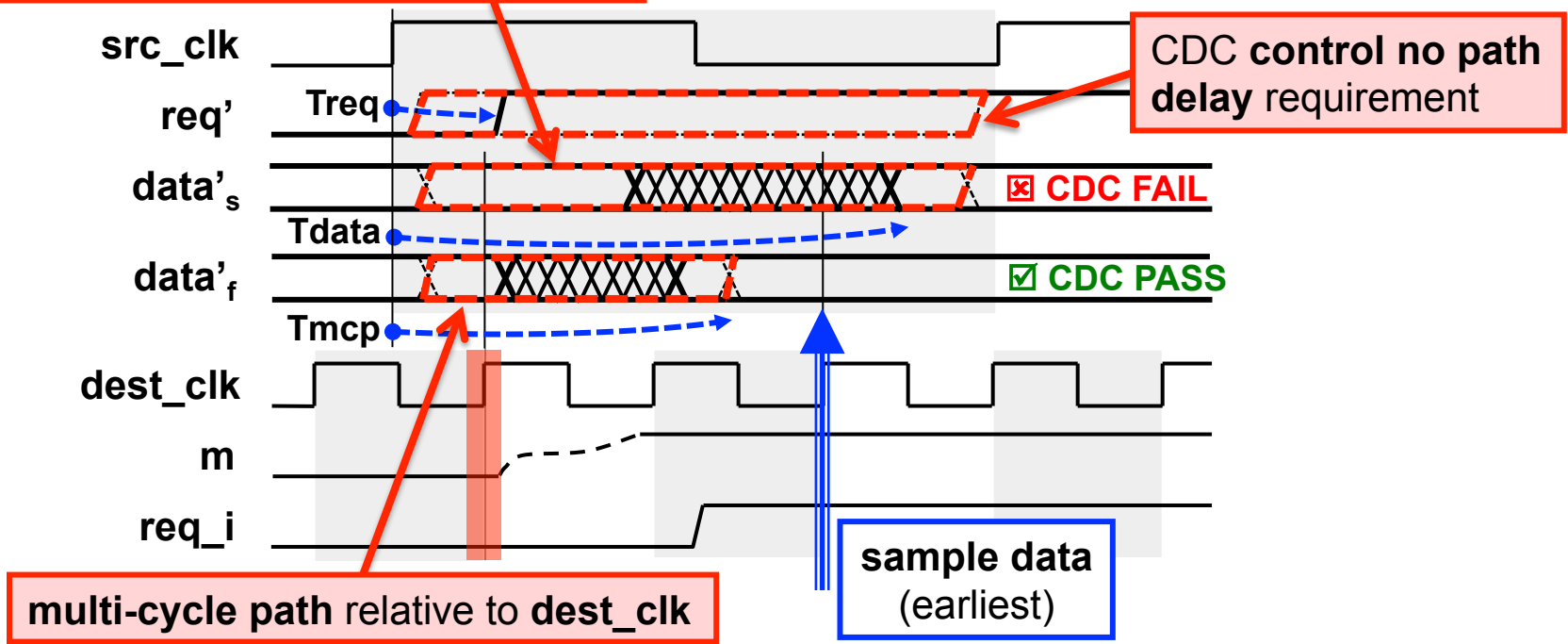Pragmatic: **MCP** of 2 x dest_clk periods (slight over-constrained if $T_{req} > Thold_2$)




$$(T_{data} + T_{ck_skew_1}) < [T_{req} + (2 \times T_{period_2}) - Thold_2]$$

Phase-Detect Synchronizers

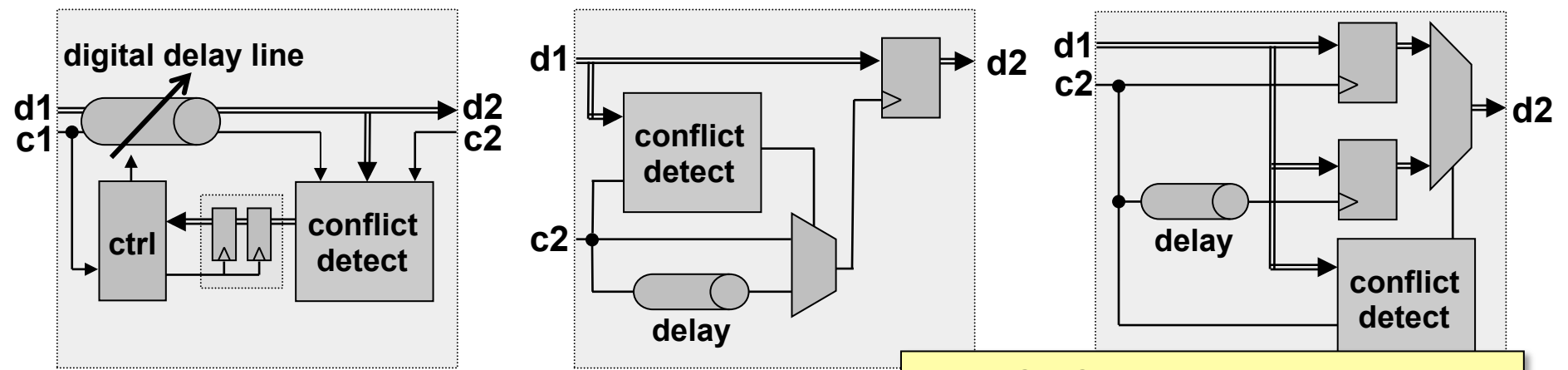

 
PHY CDC Requirements
 • sub-cycle timing on CDC data



Mesochronous
 (phase offset)

Plesiochronous
 (phase changes)

Pragmatic Solutions

 

- **Synthesize to meta-hard FF or (better) 2FF macro-cell**
 - hard to map all RTL to desired circuits (e.g. no reset, no scan)
 - manageable with internal blocks, difficult with third-party IP
- **Instantiate meta-hard FF or 2FF macro-cell into RTL**
 - compromises portability and flexibility of the RTL (RTL becomes technology and frequency dependent)
 - manageable for internal designs and technology derivatives
 - inappropriate or impossible if using or supplying third-party IP

SVA Timing Checks

- **SVA** allows *time* and *EventExpression* formal arguments
- Actual arguments are supplied by **assert property** statement

```
property p_max_time(start, stop, duration);
time start_time;
@(start)
(1, start_time = $time) |=>
@(stop)
(($time - start_time) <= duration);
endproperty
```

argument used as event expression

argument used as time variable

```
a_meta_sub_cycle: assert property (p_max_time(posedge clk, m, 300ps));
```

maximum **delay** from **posedge clk** to any **change** on **m** must be less than **300ps**

- Use **assertions** for both **RTL** and **gate-level**

Provides good **safety net** for validating **closure** on some **timing-based intent** ...

... but **be aware** that assertion **binding** to **optimized netlist** can be **non-trivial!**

Tools & Methodology

- **Gate-level CDC analysis**
 - some formal CDC analysis tools can handle GL complexity
 - add structural checks, clock-tree aware, reuse RTL intent
 - complement, but do not eradicate CDC-aware STA
- **Constraints management**
 - evolution and refinement of constraints is major issue
 - especially with multiple tool vendors in the flow
 - tools emerging to manage & validate equivalence of constraints
- **Multi-discipline CDC reviews**
 - recognize that CDC is not just an RTL problem...
 - review CDC functional operation and synchronizer physical implementation with a multi-discipline multi-talented team!

Conclusion

- Presented an **overview** of the **problem**
 - RTL verification of CDC is necessary but not sufficient
 - additional requirements need to be understood front & back-end
- Illustrated **detailed hazards** for some common synchronizers
 - intra-domain operation within synchronizers
 - inter-domain CDC requirements and relationships
- Discussed some **pragmatic solutions** & tool advances
 - anything which closes the gap is good!

Primary **goal**: raise **multi-discipline CDC awareness**

mark.litterick@verilab.com

