

# Model Validation for Mixed-Signal Verification

Carsten Wegener

Dialog Semiconductor, Germany



# Model Validation for Verification

## Overview:

- Verification target clarification by example
- Digital model of an analog cell: functionality/structure
- Functionality modeling and validation
- Structure preserving model assembly
- Case study: finding bugs by modeling
- Conclusion

# Verification target clarification

- Top-down specification
- Design phase
- Bottom-up verification

# Verification target clarification

- Top-down specification
  - **Specification model** describes intended behavior
  - Verify that block specs match system requirements
- Design phase
  
- Bottom-up verification


# Verification target clarification

- Top-down specification
  - **Specification model** describes intended behavior
  - Verify that block specs match system requirements
- Design phase
  - Adjust parameters of chosen design architecture
  - Verify performance vs. specification
- Bottom-up verification

# Verification target clarification


- Top-down specification
  - **Specification model** describes intended behavior
  - Verify that block specs match system requirements
- Design phase
  - Adjust parameters of chosen design architecture
  - Verify performance vs. specification
- Bottom-up verification
  - **Implementation model**: functionality and structure
  - Verify integration of implemented block is robust in system

# Simple input buffer example

 

# Simple input buffer example


- Specification model

 




 
# Simple input buffer example

- Specification model
  - `assign dout= por_n && PAD_IN;`
  - Verify system level interactions



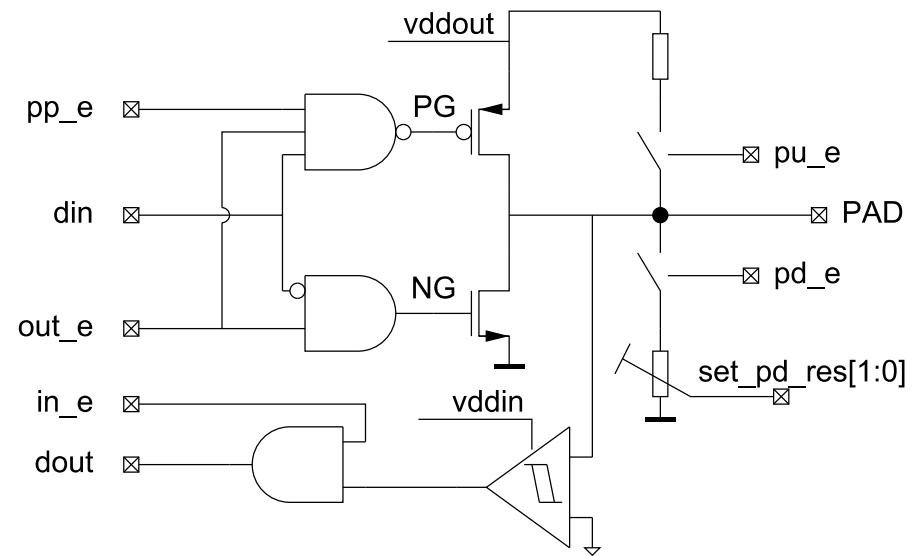
 
# Simple input buffer example

- Specification model
  - `assign dout= por_n && PAD_IN;`
  - Verify system level interactions
- Design by re-using existing cell


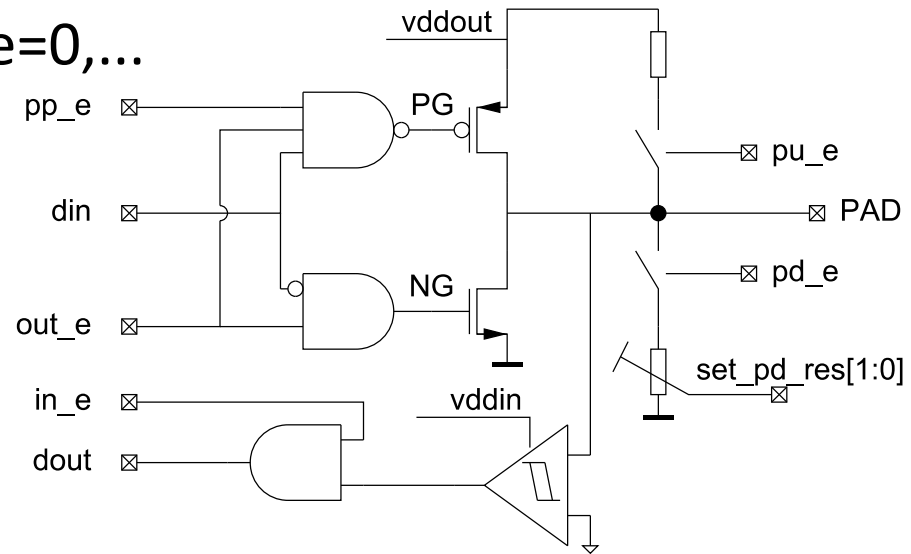 
# Simple input buffer example


- Specification model
  - `assign dout= por_n && PAD_IN;`
  - Verify system level interactions
- Design by re-using existing cell
  - Connect: `in_e=por_n, out_e=0,...`
  - Verify performance


 
# Simple input buffer example

- Specification model


- `assign dout = por_n && PAD_IN;`
- Verify system level interactions



- Design by re-using existing cell

- Connect: `in_e=por_n, out_e=0,...`
- Verify performance

- Implementation model

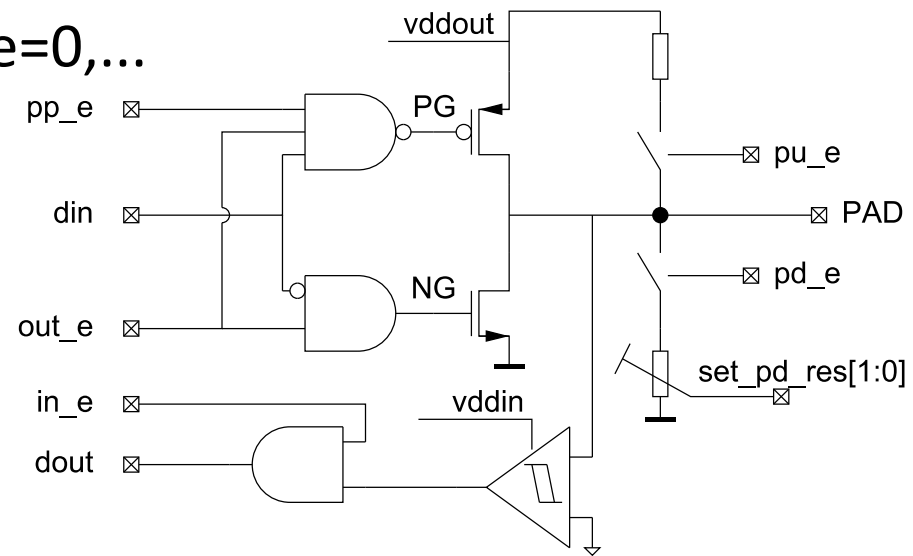

# Simple input buffer example

- Specification model



- `assign dout= por_n && PAD_IN;`
- Verify system level interactions

- Design by re-using existing cell

- Connect: `in_e=por_n, out_e=0,...`
- Verify performance

- Implementation model

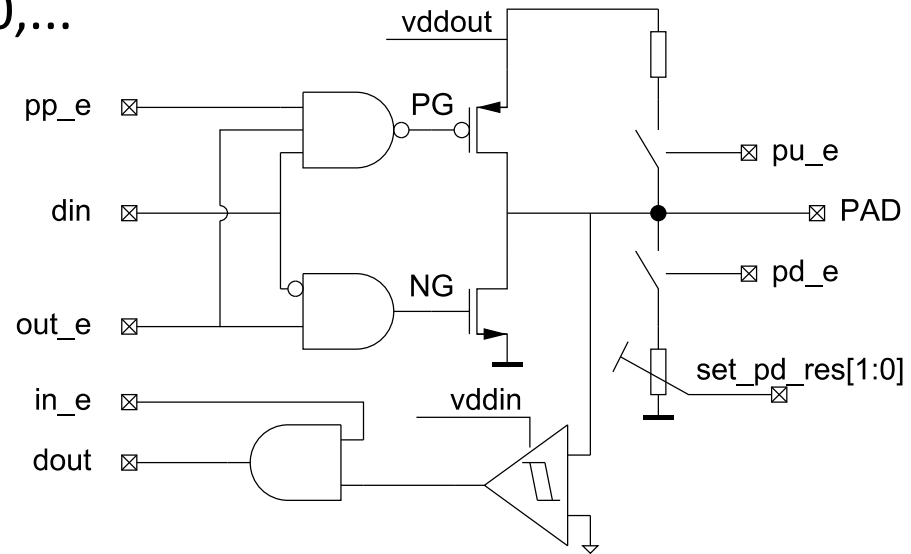 - Netlist connectivity/models
- Verify integration including supply availability




# Digital model of an analog cell

- Specification model → structure independent
  
  
  
  
  
  
  
  
  
  
- Implementation model → needs structure
 
# Digital model of an analog cell

- Specification model → structure independent

```
module NAND2 (  
  input gnd, ///  
  input vdd, ///  
  input in1,  
  input in2,  
  output out ///  
);  
assign supply_ok = gnd===1'b0 && vdd===1'b1;  
assign out = (supply_ok) ? !(in1 && in2)  
              : 1'bx;  
endmodule
```





- Implementation model → needs structure

# Digital model of an analog cell

- Specification model → structure independent

```

  module NAND2 (
  input gnd, // # TYPE=G
  input vdd, // # TYPE=P, HI=2.5
  input in1,
  input in2,
  output out // # TYPE=D, OK=DUT.supply_ok
);
assign supply_ok = gnd===1'b0 && vdd===1'b1;
assign out = (supply_ok) ? !(in1 && in2)
              : 1'bx;
endmodule
    
```



- Implementation model → needs structure





# Digital model of an analog cell

- Specification model → structure independent

```

module NAND2 (
  input gnd, // # TYPE=G
  input vdd, // # TYPE=P, HI=2.5
  input in1,
  input in2,
  output out // # TYPE=D, OK=DUT.supply_ok
);
  assign supply_ok = gnd===1'b0 && vdd===1'b1;
  assign out = (supply_ok) ? !(in1 && in2)
                  : 1'bx;
endmodule

```

  


- Implementation model → needs structure

```

module cmos_out (
  input gnd, // # TYPE=G
  input vddout, // # TYPE=P, HI=1.8
  input pg,
  input ng,
  output out // # TYPE=D, OK=DUT.out_ok
);
  assign supply_ok = gnd===1'b0 && vddout===1'b1;
  assign out = (supply_ok) ? 1'bz : 1'bx;
  assign out_ok = supply_ok && (ng ^ pg)===1'b0;
  pmos P0 (out, vddout, pg);
  nmos N0 (out, gnd, ng);
endmodule

```

 



© Accellera Systems Initiative

# Digital model of an analog cell

- Specification model → structure independent


```

  module NAND2 (
  input gnd, // # TYPE=G
  input vdd, // # TYPE=P, HI=2.5
  input in1,
  input in2,
  output out // # TYPE=D, OK=DUT.supply_ok
);
assign supply_ok = gnd===1'b0 && vdd===1'b1;
assign out = (supply_ok) ? !(in1 && in2)
                : 1'bx;
endmodule
    
```



- Implementation model → needs structure

 - No spec for vddout up and down
- Structure → well-defined out=0 for en=0, dvdd > vddout=0 → 1 → 0



```



module cmos_out (
  input gnd, // # TYPE=G
  input vddout, // # TYPE=P, HI=1.8
  input pg,
  input ng,
  output out // # TYPE=D, OK=DUT.out_ok
);
assign supply_ok = gnd===1'b0 && vddout===1'b1;
assign out = (supply_ok) ? 1'bz : 1'bx;
assign out_ok = supply_ok && (ng ^ pg)===1'b0;
pmos P0 (out, vddout, pg);
nmos N0 (out, gnd, ng);
endmodule
    
```

# Digital model of an analog cell

- Specification model → structure independent


```

  module NAND2 (
  input gnd, // # TYPE=G
  input vdd, // # TYPE=P, HI=2.5
  input in1,
  input in2,
  output out // # TYPE=D, OK=DUT.supply_ok
);
assign supply_ok = gnd===1'b0 && vdd===1'b1;
assign out = (supply_ok) ? !(in1 && in2)
               : 1'bx;
endmodule
    
```



- Implementation model → needs structure

 - No spec for vddout up and down
- Structure → well-defined out=0 for en=0, dvdd > vddout=0 → 1 → 0



```



module cmos_out (
  input gnd, // # TYPE=G
  input vddout, // # TYPE=P, HI=1.8
  input pg,
  input ng,
  output out // # TYPE=D, OK=DUT.out_ok
);
assign supply_ok = gnd===1'b0 && (vddout===1'b1;
assign out = (supply_ok) ? 1'bz : 1'bx; || ng && pg)
assign out_ok = supply_ok && (ng ^ pg)===1'b0;
pmos P0 (out, vddout, pg);
nmos N0 (out, gnd, ng);
endmodule
    
```

# Digital model of an analog cell

- Specification model → structure independent


```

  module NAND2 (
  input gnd, // # TYPE=G
  input vdd, // # TYPE=P, HI=2.5
  input in1,
  input in2,
  output out // # TYPE=D, OK=DUT.supply_ok
);
  assign supply_ok = gnd===1'b0 && vdd===1'b1;
  assign out = (supply_ok) ? !(in1 && in2)
                : 1'bx;
endmodule
    
```



- Implementation model → needs structure

 
- No spec for vddout up and down
- Structure →  $ng=pg=x \rightarrow out=x$   
for  $en=0$ ,  $dvdd > vddout=0 \rightarrow 1 \rightarrow 0$



```

module cmos_out (
  input gnd, // # TYPE=G
  input vddout, // # TYPE=P, HI=1.8
  input pg,
  input ng,
  output out // # TYPE=D, OK=DUT.out_ok
);
  assign supply_ok = gnd===1'b0 && (vddout===1'b1;
  assign out = (supply_ok) ? 1'bz : 1'bx; || ng && pg)
  assign out_ok = supply_ok && (ng ^ pg)===1'b0;
  pmos P0 (out, vddout, pg);
  nmos N0 (out, gnd, ng);
endmodule
    
```

 
# Functionality modeling and validation: The Importance of Being Earnest



```
module NAND2 (  
  input gnd, //# TYPE=G  
  input vdd, //# TYPE=P, HI=2.5  
  input in1,  
  input in2,  
  output out //# TYPE=D, OK=DUT.supply_ok  
);  
  assign supply_ok =  
    gnd===1'b0 || (in1===1'b0||in2===1'b0)  
    && vdd===1'b1 || ({in1,in2}===2'b11);  
  assign out = (supply_ok) ? !(in1 && in2)  
    : 1'bx;  
endmodule
```
 
# Functionality modeling and validation: The Importance of Being Earnest



- Validation: stimulate inputs and compare response vs. expectation and transistor implementation



```
module NAND2 (  
    input gnd, //# TYPE=G  
    input vdd, //# TYPE=P, HI=2.5  
    input in1,  
    input in2,  
    output out //# TYPE=D, OK=DUT.supply_ok  
);  
    assign supply_ok =  
        gnd===1'b0 || (in1===1'b0||in2===1'b0)  
        && vdd===1'b1 || ({in1,in2}===2'b11);  
    assign out = (supply_ok) ? !(in1 && in2)  
        : 1'bx;  
endmodule
```
  
# Functionality modeling and validation: The Importance of Being Earnest

- Validation: stimulate inputs and compare response vs. expectation and transistor implementation



PMOS:  
25/1  
NMOS:  
10/1



```

module NAND2 (
  input gnd, //# TYPE=G
  input vdd, //# TYPE=P, HI=2.5
  input in1,
  input in2,
  output out //# TYPE=D, OK=DUT.supply_ok
);
  assign supply_ok =
    gnd===1'b0 || (in1===1'b0||in2===1'b0)
    && vdd===1'b1 || ({in1,in2}===2'b11);
  assign out = (supply_ok) ? !(in1 && in2)
    : 1'bx;
endmodule

```
  
# Functionality modeling and validation: The Importance of Being Earnest


- Validation: stimulate inputs and compare response vs. expectation and transistor implementation
- Describe expectation with Wavedrom stim\_pass=1



```

module NAND2 (
  input gnd, //# TYPE=G
  input vdd, //# TYPE=P, HI=2.5
  input in1,
  input in2,
  output out //# TYPE=D, OK=DUT.supply_ok
);
  assign supply_ok =
    gnd===1'b0 || (in1===1'b0||in2===1'b0)
    && vdd===1'b1 || ({in1,in2}===2'b11);
  assign out = (supply_ok) ? !(in1 && in2)
    : 1'bx;
endmodule



```

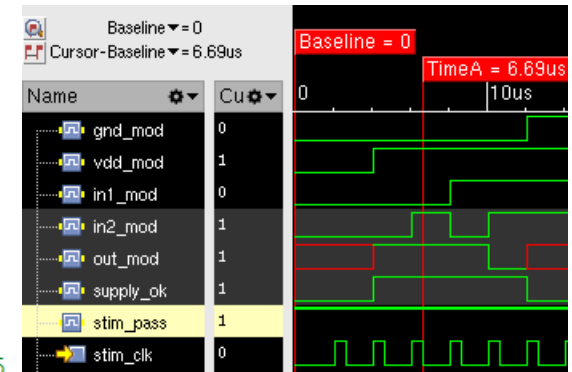


 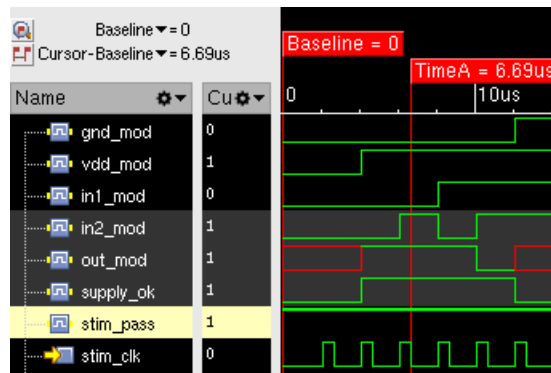
# Functionality modeling and validation: Expectations beyond the obvious

- Validation: stimulate inputs and compare response
- Describe expectation with Wavedrom → stim\_pass=1





```

module NAND2 (
  input gnd, //# TYPE=G
  input vdd, //# TYPE=P, HI=2.5
  input in1,
  input in2,
  output out //# TYPE=D, OK=DUT.supply_ok
);
  assign supply_ok =
    gnd===1'b0 || (in1===1'b0||in2===1'b0)
    && vdd===1'b1 || ({in1,in2}===2'b11);
  assign out = (supply_ok) ? !(in1 && in2)
    : 1'bx;
endmodule

```
 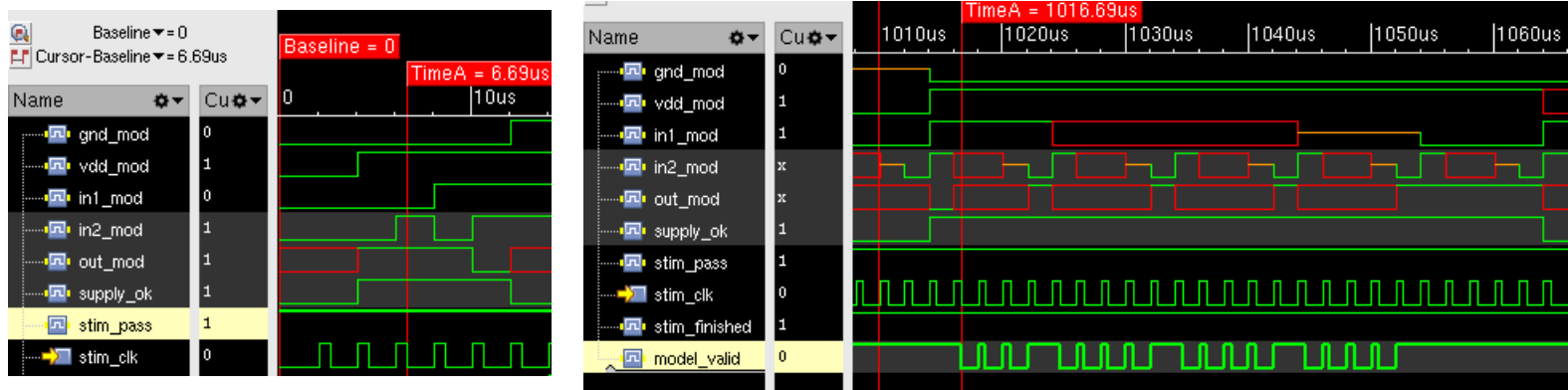
# Functionality modeling and validation: Expectations beyond the obvious

- Validation: stimulate inputs and compare response
- Describe expectation with Wavedrom → stim\_pass=1
- Apply all stimulus combinations → model\_valid=1





```

input in1,
input in2,
output out //# TYPE=D, OK=DUT.supply_ok
);
assign supply_ok =
    gnd===1'b0 || (in1===1'b0||in2===1'b0)
    && vdd===1'b1 || ({in1,in2}===2'b11);
assign out = (supply_ok) ? !(in1 && in2)
                : 1'bx;
endmodule

```
 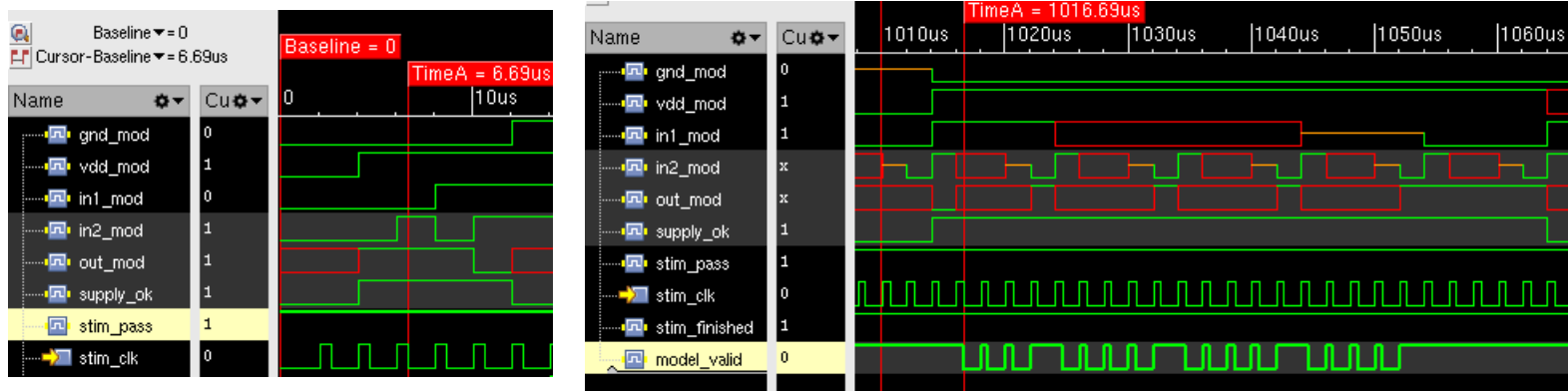
# Functionality modeling and validation: Expectations beyond the obvious

- Validation: stimulate inputs and compare response
- Describe expectation with Wavedrom → stim\_pass=1
- Apply all stimulus combinations → model\_valid=1 → Fix model!




```

input in1,
input in2,
output out //# TYPE=D, OK=DUT.supply_ok
);
assign supply_ok =
    ( gnd===1'b0 || (in1===1'b0||in2===1'b0) )
    && vdd===1'b1 || ({in1,in2}===2'b11) ;
assign out = (supply_ok) ? !(in1 && in2)
               : 1'bx;
endmodule
    
```

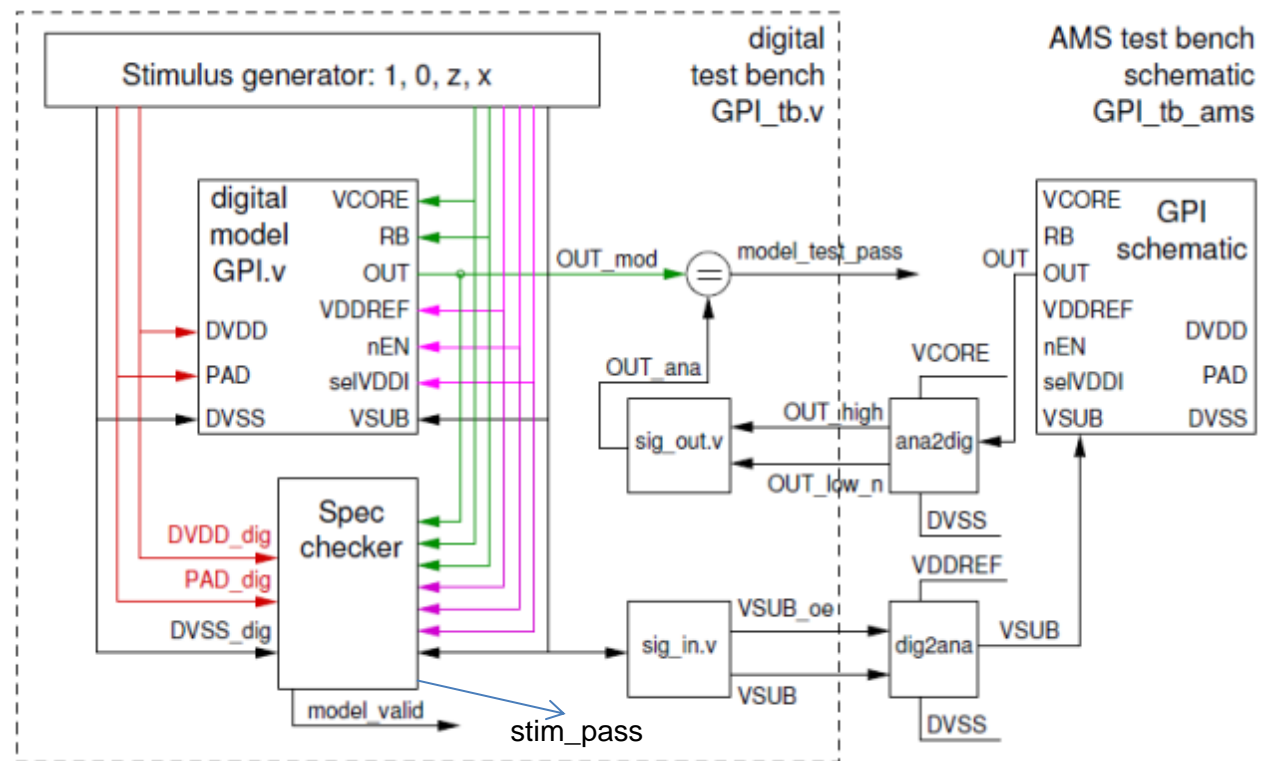
# Functionality modeling and validation: Expect to match schematic

- Validation: stimulate inputs and compare response
- Sign-off: stim\_pass, model\_valid, model\_test\_pass=1



 
# Functionality modeling and validation: Expect to match schematic

- Validation: stimulate inputs and compare response
- Sign-off: stim\_pass, model\_valid, model\_test\_pass=1
- Script-based AMS test bench generation



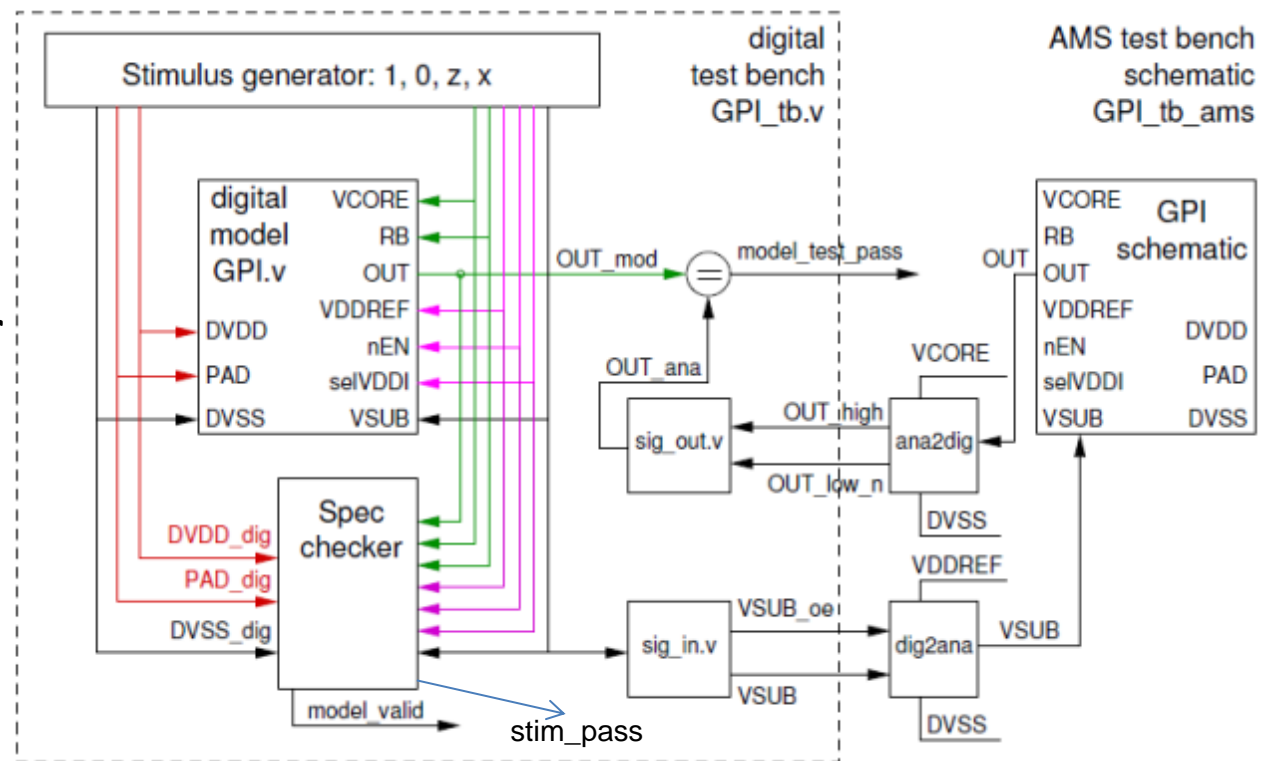
# Functionality modeling and validation: Expect to match schematic

- Validation: stimulate inputs and compare response
- Sign-off: `stim_pass, model_valid, model_test_pass=1`
- Script-based AMS test bench generation
- Regression over all models



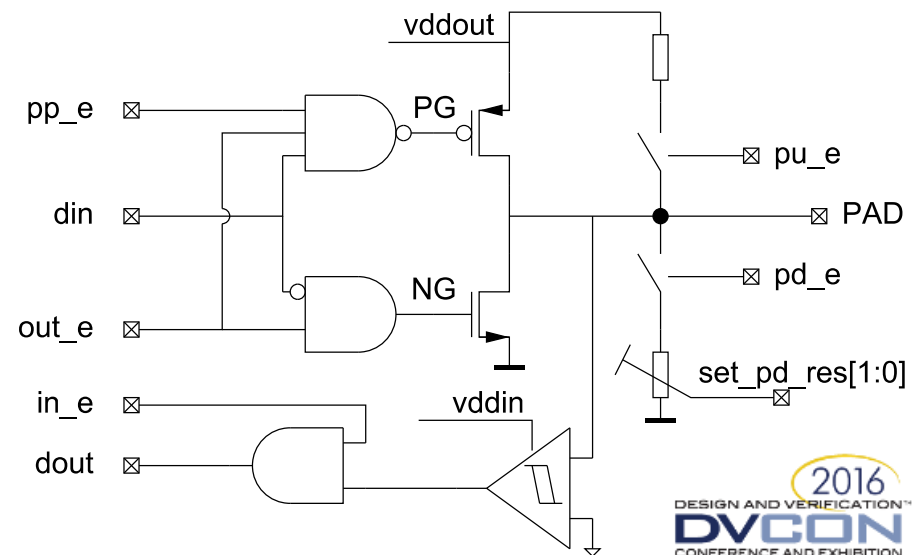
# Structure preserving model assembly

- Assume models for low-level analog structures


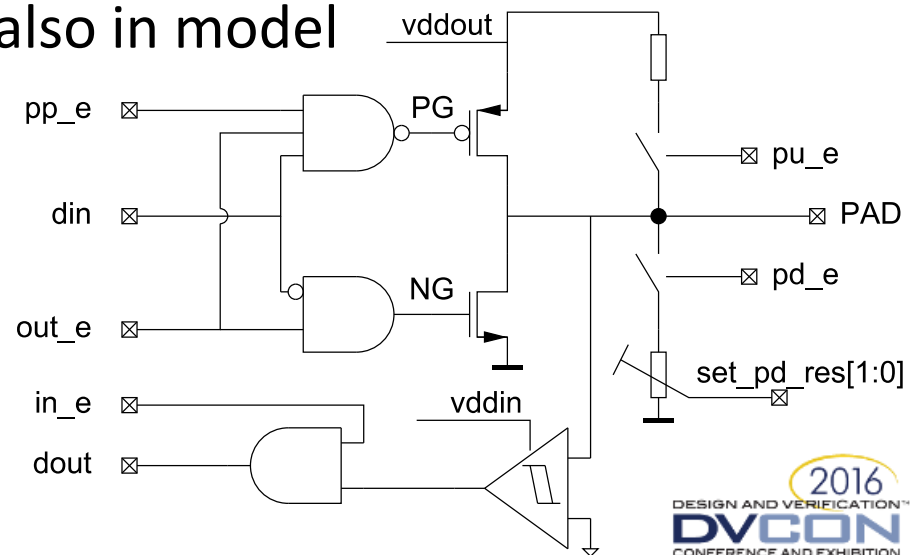
# Structure preserving model assembly

- Assume models for low-level analog structures
- Use netlister for model assembly
  - Accommodate late design changes
  - Re-use sub-blocks and validated models
  - Implementation model valid by construction
  - Structural design bugs are also in model







# Structure preserving model assembly

- Assume models for low-level analog structures
- Use netlister for model assembly
  - Accommodate late design changes
  - Re-use sub-blocks and validated models
  - Implementation model valid by construction
  - Structural design bugs are also in model

- Example: IO cell designs

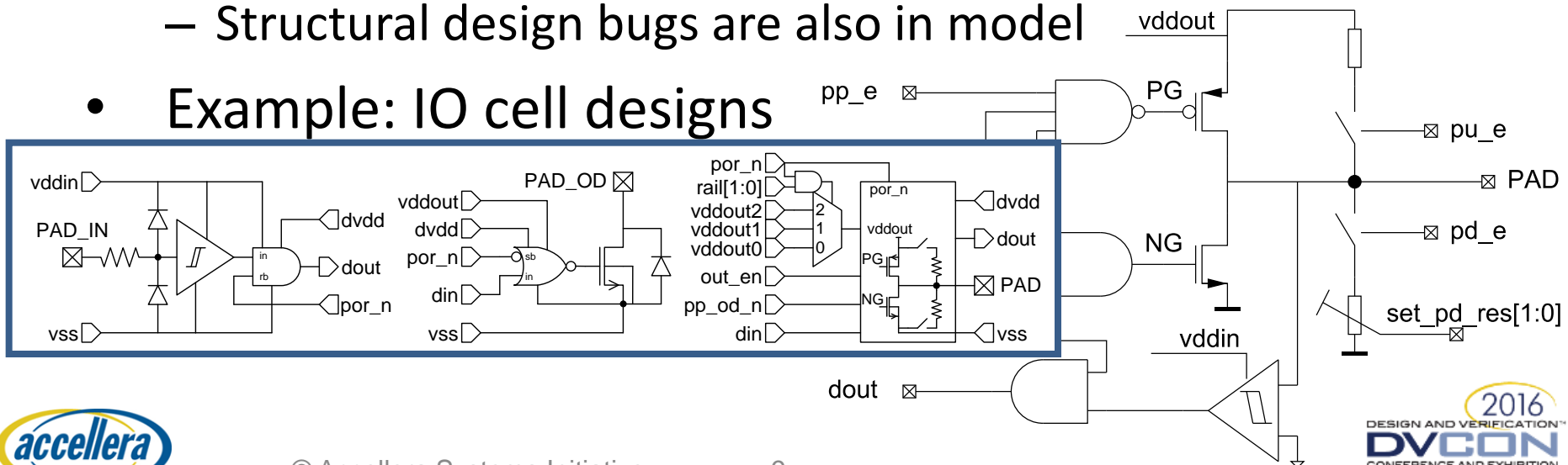


# Case study: Simple input buffer

 
 
# Case study: Simple input buffer



- Specification model

- `assign dout = por_n && PAD_IN;`
- Verify system level interactions



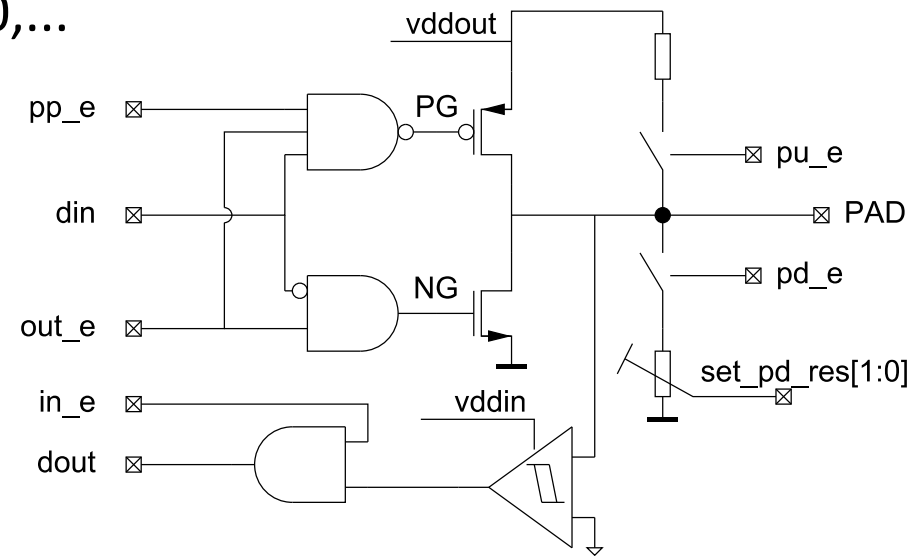
 
# Case study: Simple input buffer

- Specification model
  - `assign dout= por_n && PAD_IN;`
  - Verify system level interactions
- Design by re-using existing cell
  - Connect: `in_e=por_n, pu_e=0,...`


  
# Case study: Simple input buffer

- Specification model
  - `assign dout= por_n && PAD_IN;`
  - Verify system level interactions
- Design by re-using existing cell
  - Connect: `in_e=por_n, pu_e=0,...`
  - Remove output stage



# Case study: Simple input buffer

- Specification model



- `assign dout = por_n && PAD_IN;`
- Verify system level interactions

- Design by re-using existing cell

- Connect: `in_e = por_n, pu_e = 0, ...`
- Remove output stage

- Implementation model

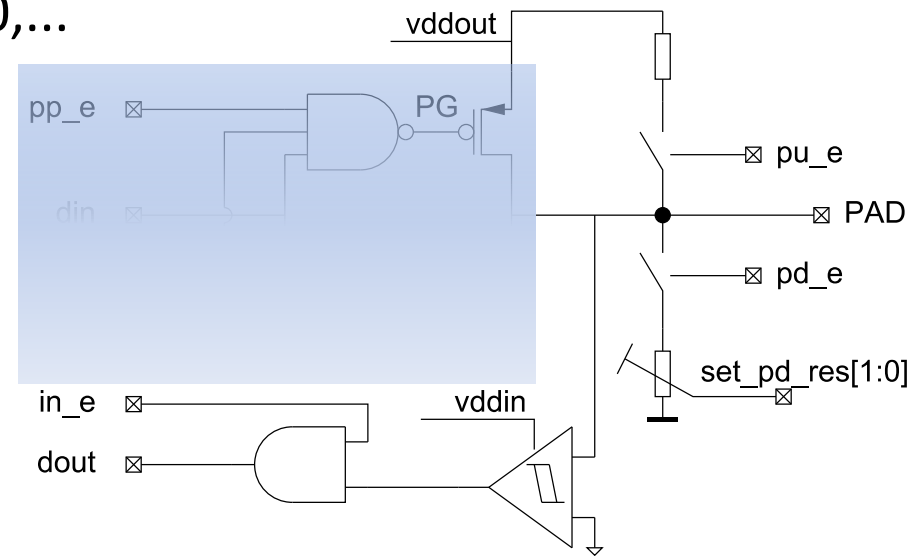 - Netlist connectivity/models
- Verify integration including supply availability



# Case study: Simple input buffer

- Specification model



- `assign dout = por_n && PAD_IN;`
- Verify system level interactions

- Design by re-using existing cell

- Connect: `in_e = por_n, pu_e = 0, ...`
- Remove output stage

- Implementation model


 
 
- Netlist connectivity/models
- Verify integration including supply availability




Validation exhibits `PAD_IN=1'bx`
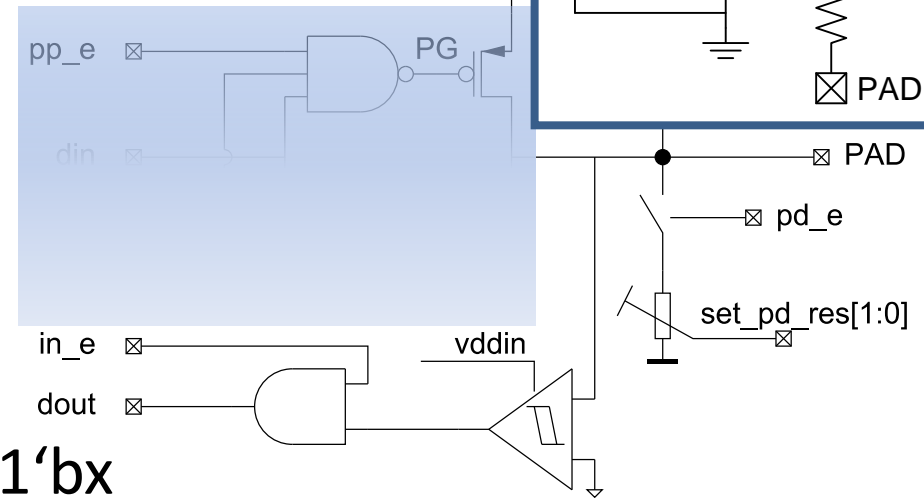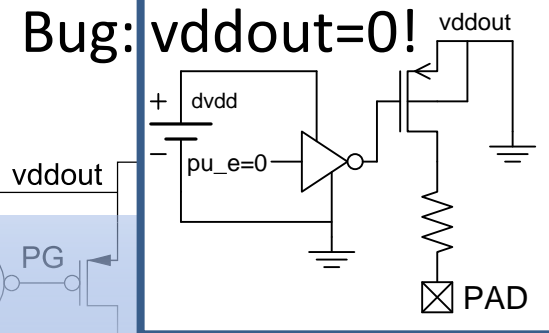 
# Case study: Simple input buffer

- Specification model
  - `assign dout= por_n && PAD_IN;`
  - Verify system level interactions
- Design by re-using existing cell
  - Connect: `in_e=por_n, pu_e=0,...`
  - Remove output stage
- Implementation model
  - Netlist connectivity/models
  - Verify integration including supply availability



 Validation exhibits PAD\_IN=1'bx



# Conclusions

- Distinguish specification and implementation models  
→ different purpose, different construction

# Conclusions

- Distinguish specification and implementation models  
→ different purpose, different construction
- Validate models against expectation and schematics  
→ need script-based test bench generation

# Conclusions

- Distinguish specification and implementation models
  - different purpose, different construction
- Validate models against expectation and schematics
  - need script-based test bench generation
- For modeling and validation:
  - Keep models small (many inputs, but **one** output)
  - Signal flow from inputs to output; no feedback to input
  - Design hierarchy supports netlist-based model assembly

# Conclusions

- Distinguish specification and implementation models
  - different purpose, different construction
- Validate models against expectation and schematics
  - need script-based test bench generation
- For modeling and validation:
  - Keep models small (many inputs, but **one** output)
  - Signal flow from inputs to output; no feedback to input
  - Design hierarchy supports netlist-based model assembly
- Event-driven model also finds bugs in analog design

# Conclusions

- Distinguish specification and implementation models  
→ different purpose, different construction
- Validate models against expectation and schematics  
→ need script-based test bench generation
- For modeling and validation:
  - Keep models small (many inputs, but **one** output)
  - Signal flow from inputs to output; no feedback to input
  - Design hierarchy supports netlist-based model assembly
- Event-driven model also finds bugs in analog design
- Model is formulation of circuit understanding

# Conclusions

- Distinguish specification and implementation models  
→ different purpose, different construction
- Validate models against expectation and schematics  
→ need script-based test bench generation
- For modeling and validation:
  - Keep models small (many inputs, but **one** output)
  - Signal flow from inputs to output; no feedback to input
  - Design hierarchy supports netlist-based model assembly
- Event-driven model also finds bugs in analog design
- Model is formulation of circuit understanding