

Real Number Modeling for RF Circuits

Jakub Dudek, ADI US

Joshua Nekl, ADI Ireland

Keith O'Donoghue, ADI Ireland



Outline


- Motivation
- TX Path Models
- RX Path Models
- Performance
- Validation
- Conclusion

Motivation


Full chip model of a RF SoC

- Test case development and debug
- Horizontal re-use: Eval (PSS!)
- Firmware development and debug
- Not suited for:
 - RF performance (noise, linearity, etc...)
 - Analog performance (current draw, brown outs, etc...)


RF Front End

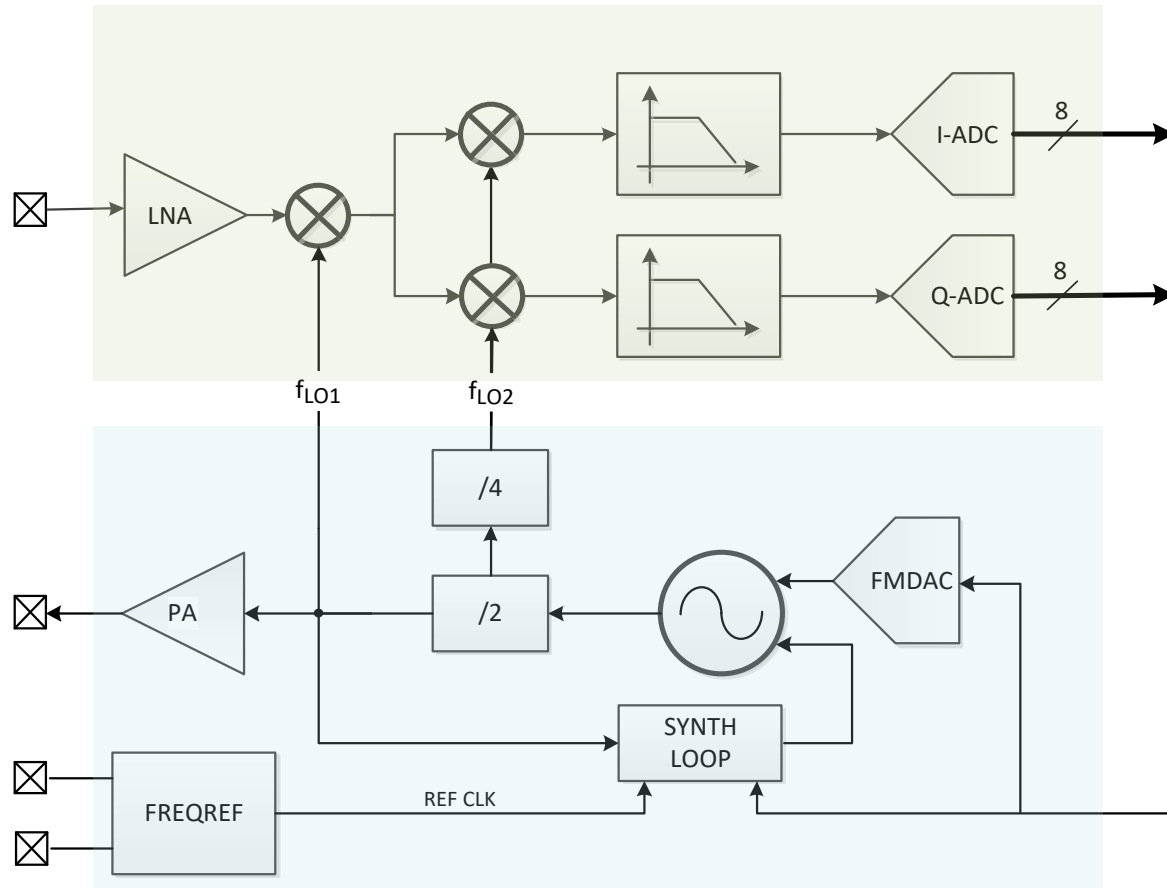


TX Path

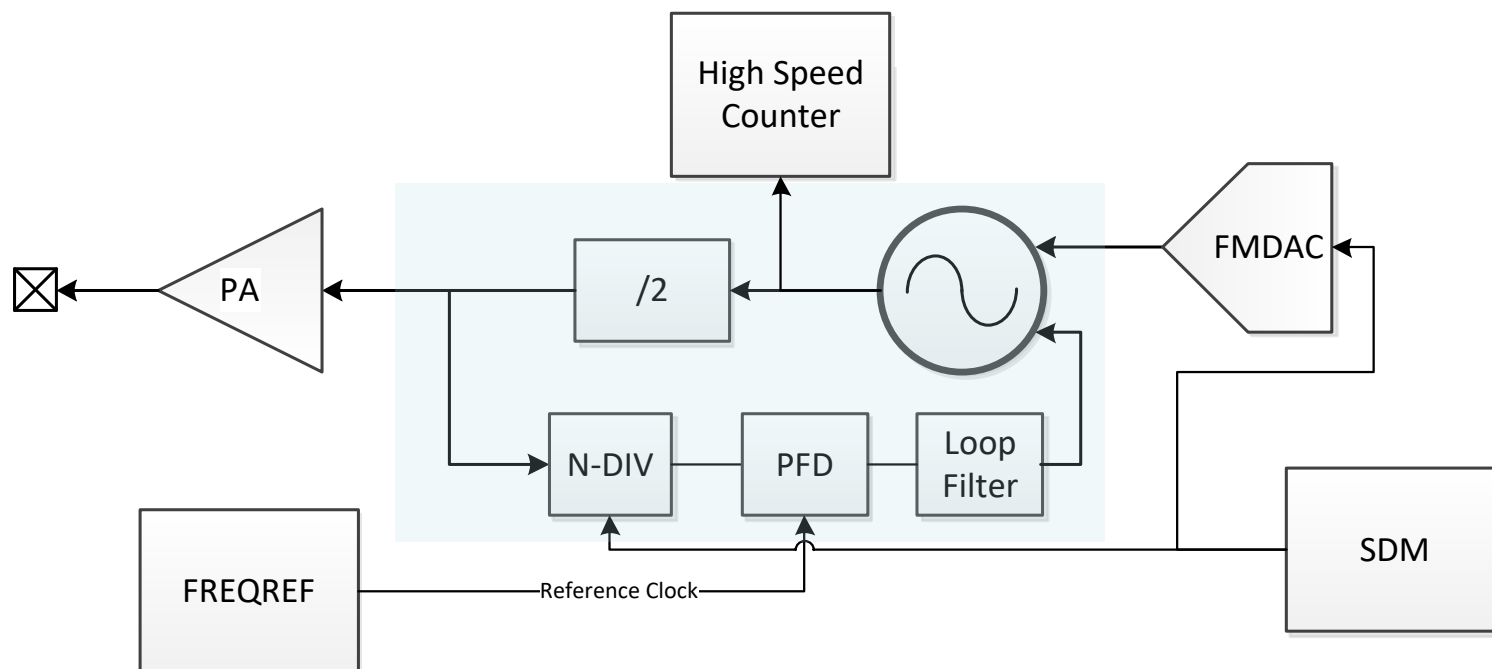

PLL

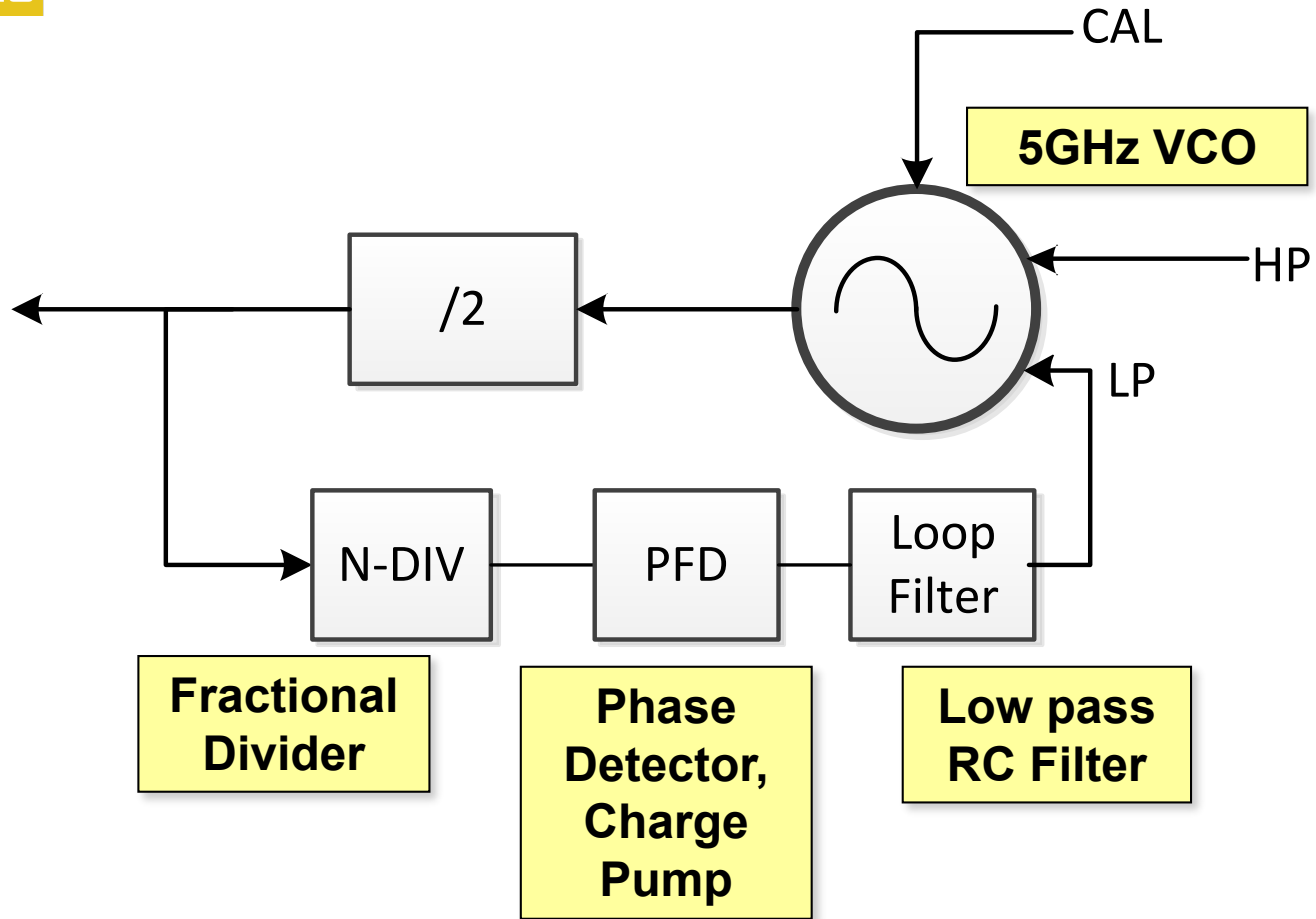

 - VCO inputs:
 - loop filter port
 - modulation port
 - calibration codes



```
assign f_vco = fc + kv_lp * (vtune_lp-0.6) +
              kv_hp * (vtune_hp_p-vtune_hp_m);
assign hperiod = (1s/f_vco)/2.0;
```

```
always begin
    wait(pwr_ok);
    #hperiod vco = !vco & pwr_ok;
end
```

Phase Detector/Charge Pump

```
always @(posedge ref_clk or negedge rst)
begin
  if(!rst) begin
    pup = 1'b0;
  end else if(pdown) begin
    pdown <= 1'b0;
  end else begin
    pup <= 1'b1;
  end
end
```


```
always @(posedge div_clk or negedge rst)
begin
  if(!rst) begin
    pdown = 1'b0;
  end else if(pup) begin
    pup <= 1'b0;
  end else begin
    pdown <= 1'b1;
  end
end
```

```
always @(posedge pup)
  pup_time = $realtime;



always @(posedge pdown)
  pdn_time = $realtime;

always @(negedge pup)
  filter(($realtime-pup_time)*Icp);

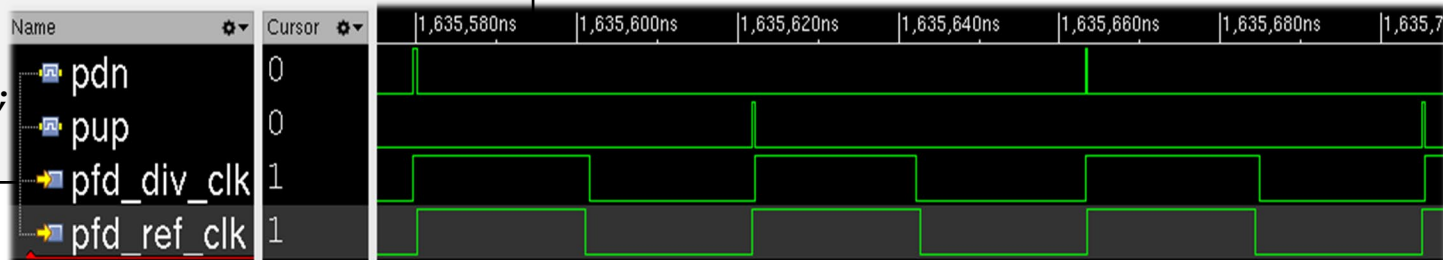always @(negedge pdown)
  filter((pdn_time-$realtime)*Icp);
```



Loop Filter

  

```

t /= 1s;

// sanity check
t = min(t, +Txtal);
t = max(t, -Txtal);


// integrate charge pump
// current onto C2
Vc2 += Qin/C2;

// compute currents, I=V/R
Ir1 = (Vc2-Vc1)/R1;
Ir2 = (Vc2-Vc3)/R2;
Ir3 = (Vc3-Vc4)/R3;



// compute voltages: V=I*t/C
Vc1 += Ir1*Txtal/C1;
Vc2 -= (Ir1+Ir2)*Txtal/C2;
Vc3 += (Ir2-Ir3)*Txtal/C3;
Vc4 += Ir3*Txtal/C4;


Vc2 = min(Vc2, Vdd);
Vc2 = max(Vc2, 0);
    
```

Lock example

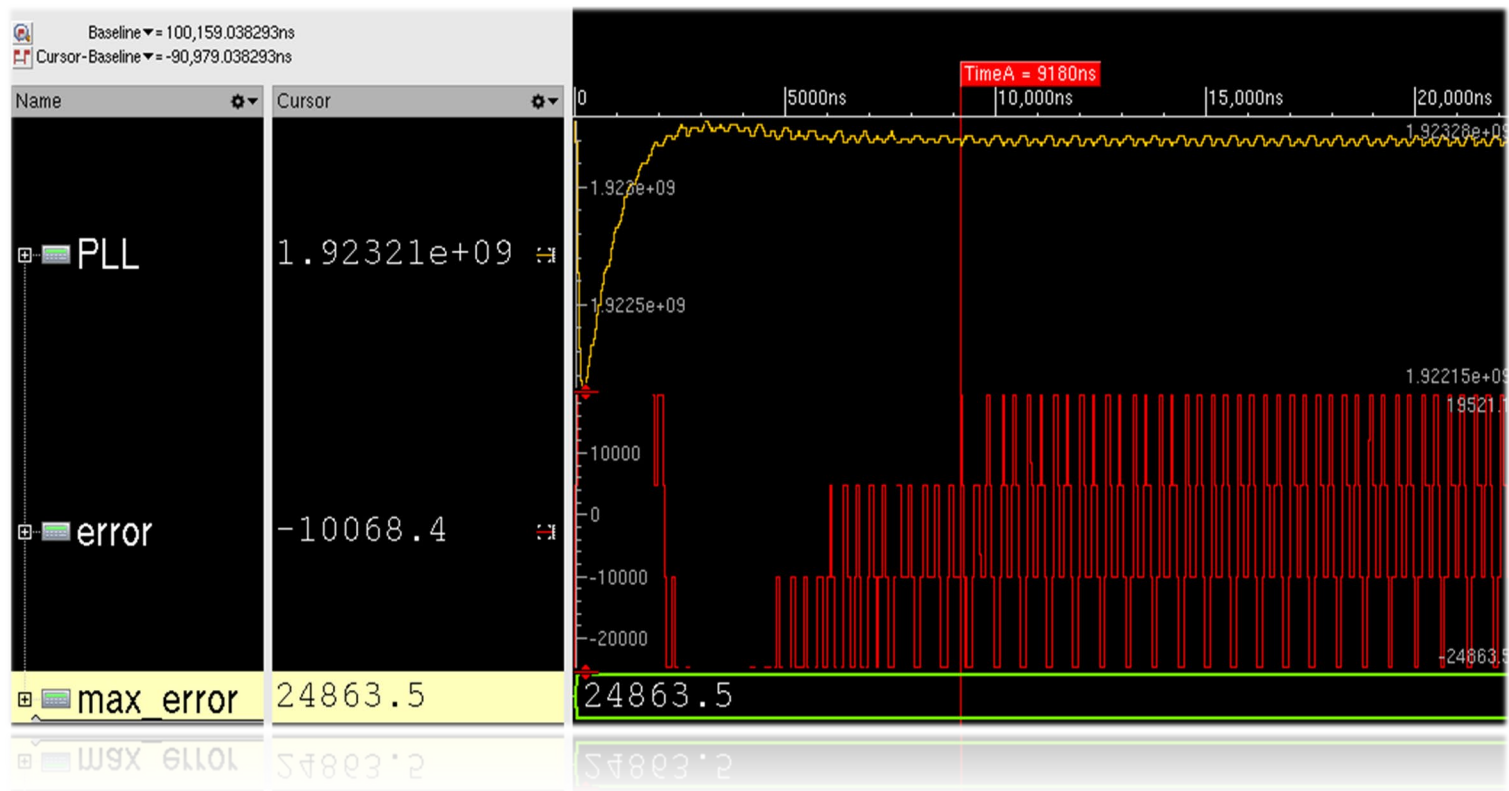


Modulation

 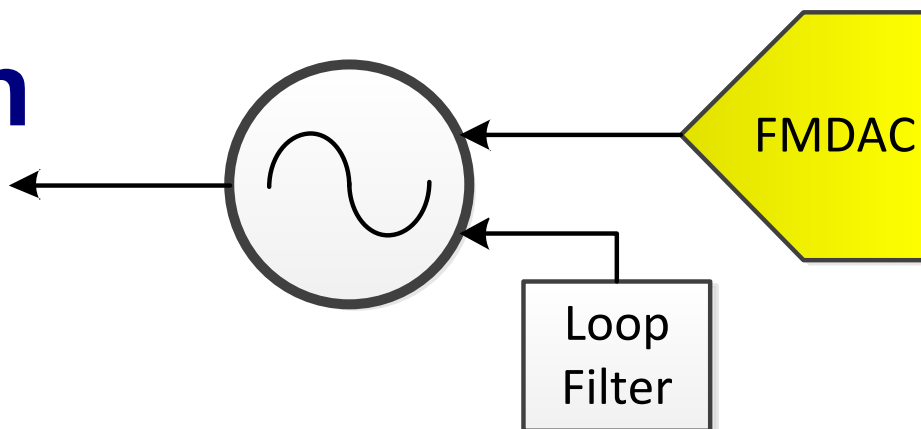


 

RF Stimulus

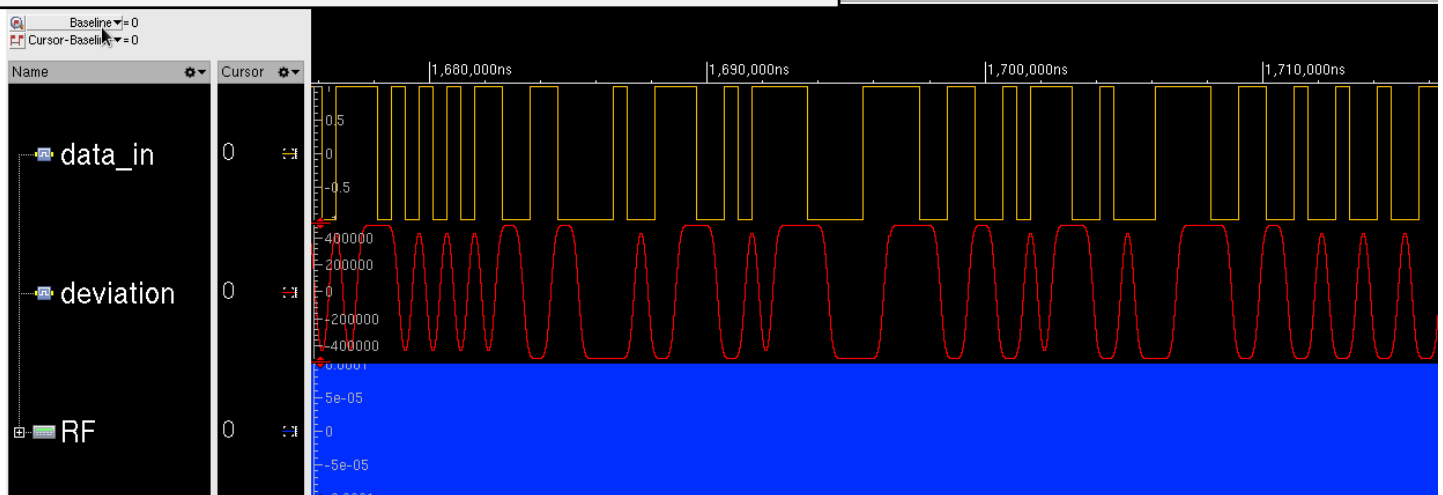
```
rf_tstep = 1/((fc+f_err+fdev+fdrift)/2);  
task gen_rf;  
    forever begin  
        wait(rf_tstep > 0);  
        #(rf_tstep *1s);  
        vif.rf_r = (vif.rf_r<0) ? amp:-amp;  
    end  
endtask
```



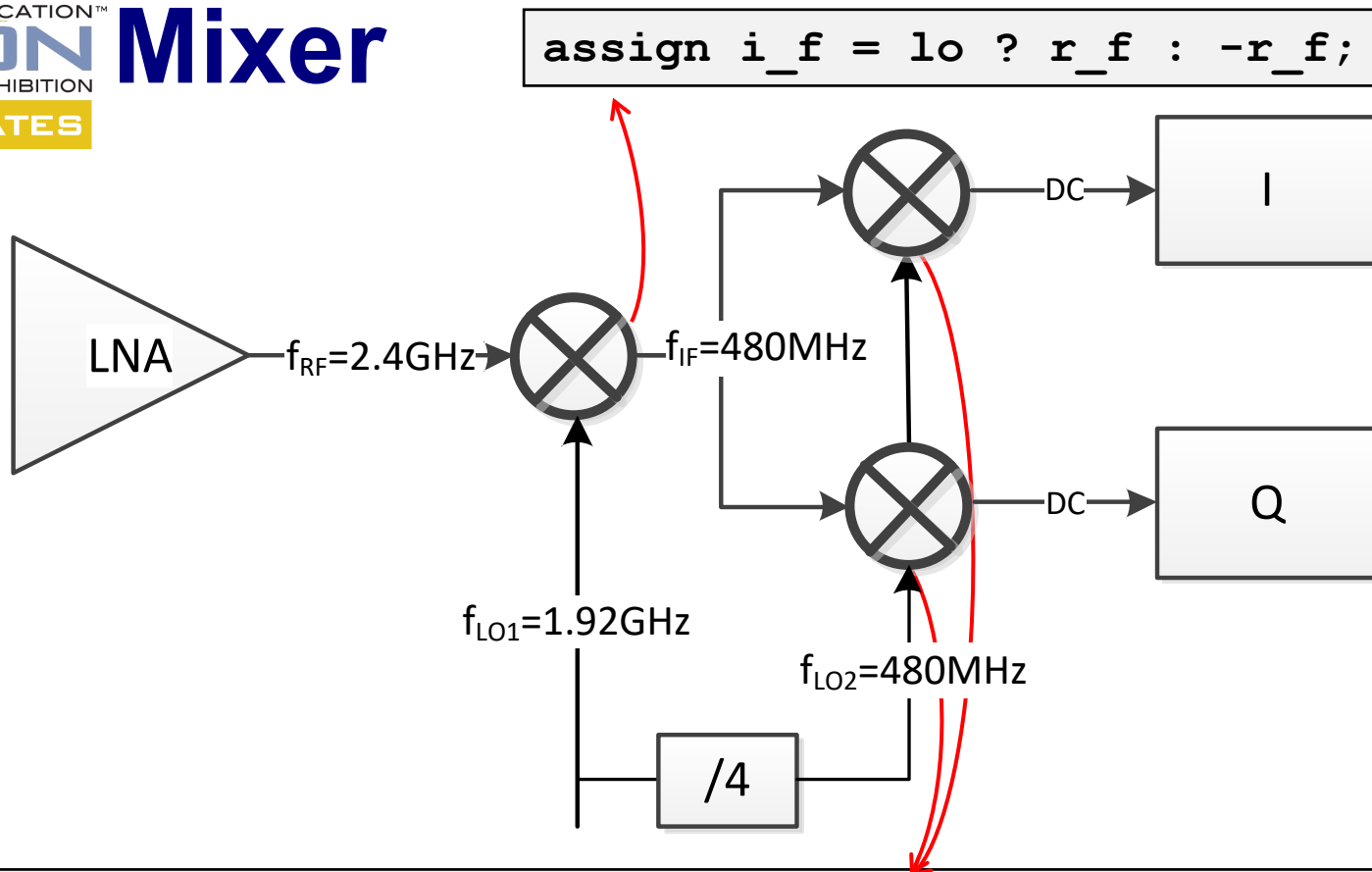


```
assign i_f = lo ? r_f : -r_f;
```
 
```
assign I = lo_cos_p ? +i_f : lo_cos_n ? -i_f : 0;
assign Q = lo_sin_p ? +i_f : lo_sin_n ? -i_f : 0;
```



Mixer Bandwidth

 - Specification
 - RF mixer: 1st order cutoff at 1GHz
 - IF mixer: 1st order cutoff at 10MHz





$$\omega_c = 2\pi \frac{f_c}{f_s} = 2\pi f_c T_s$$

$$\beta = -1 + \cos(\omega_c) + \sqrt{(\cos(\omega_c) - 3)(\cos(\omega_c) - 1)}$$


$$\beta \cong \omega_c \text{ for } f_c \ll f_s$$

Mixer Bandwidth

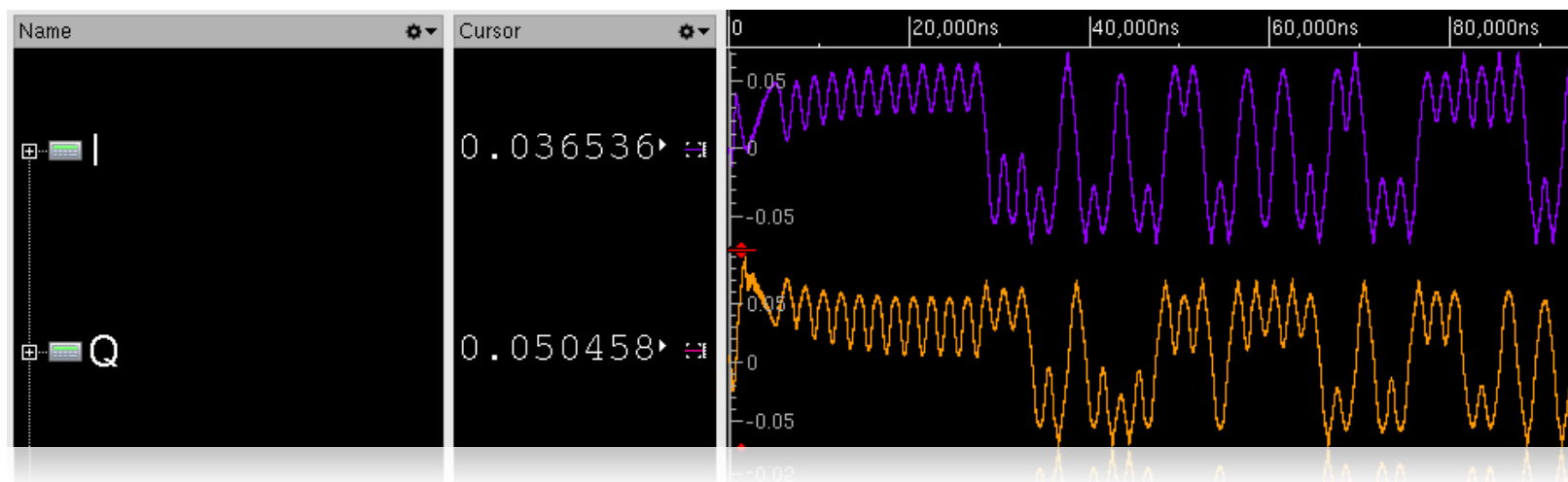 

Baseband Filter

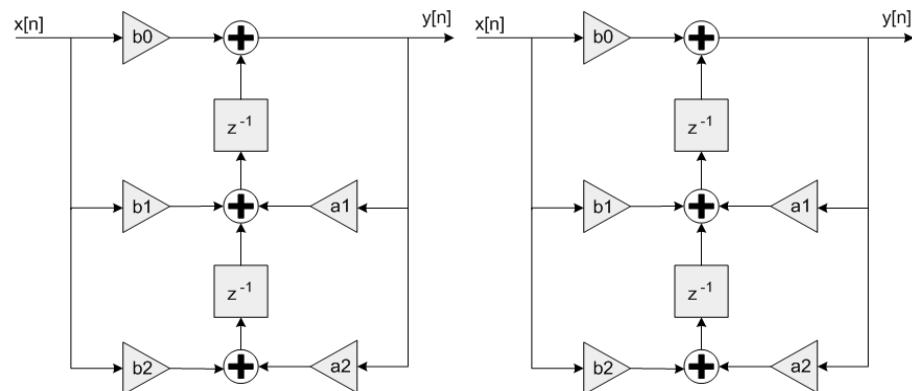- BBF synthesized using bilinear transform
- Matlab function:
 - `butter()` => Butterworth filter
 - `tf2sos()` => biquads



```
// first biquad
always@(posedge clk) begin
    x01 <= in0*b01 - out0*a01 + x02;
    x02 <= in0*b02 - out0*a02;
end


always@(x01)
    out0 = (in0*b00+x01);
assign in1 = out0;

// second biquad
always@(posedge clk) begin
    x11 <= in1*b11 - out1*a11 + x12;
    x12 <= in1*b12 - out1*a12;
end

always@(x11)
    out1 = (in1*b10+x11);

assign out = g*out1;
```


Baseband Filter Performance

 

BBF Sampling Rate

Non uniform sampling at output of mixer
Some very high frequency components


163GHz!

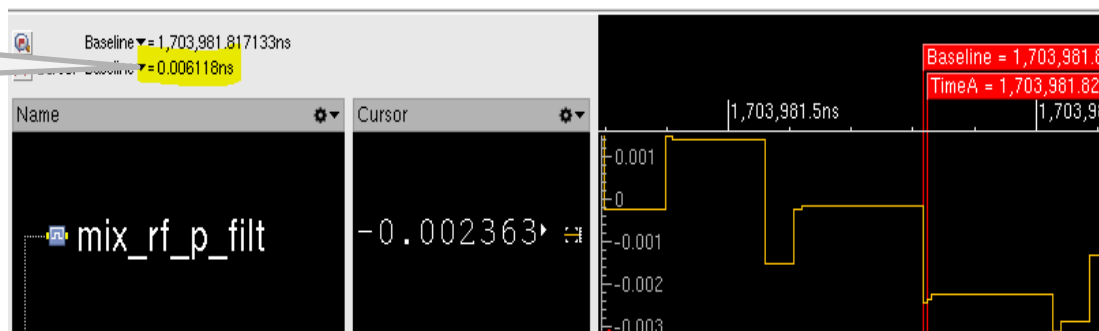


- Higher BBF sampling rate
 - better accuracy
 - precision loss in coefficients
 - slower simulation

Simulation Performance

RX

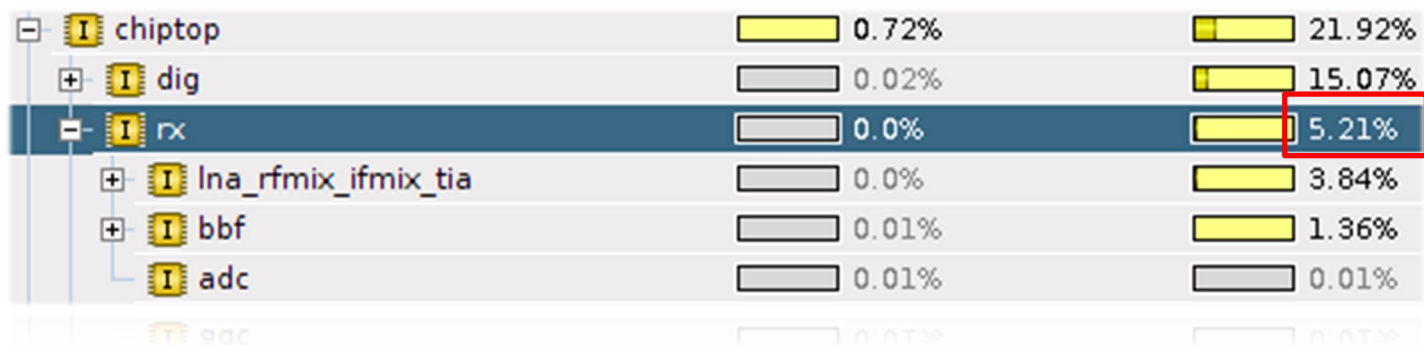

TX

 


Simulation Performance

RX

[-] I chiptop	0.07%	51.9%
[+] I dig	0.12%	28.06%
[-] I rx	0.0%	19.54%
[+] I lna_rfmix_ifmix_tia	0.0%	16.64%
[+] I bbf	0.0%	2.86%
I adc	0.04%	0.04%

Simulation Performance

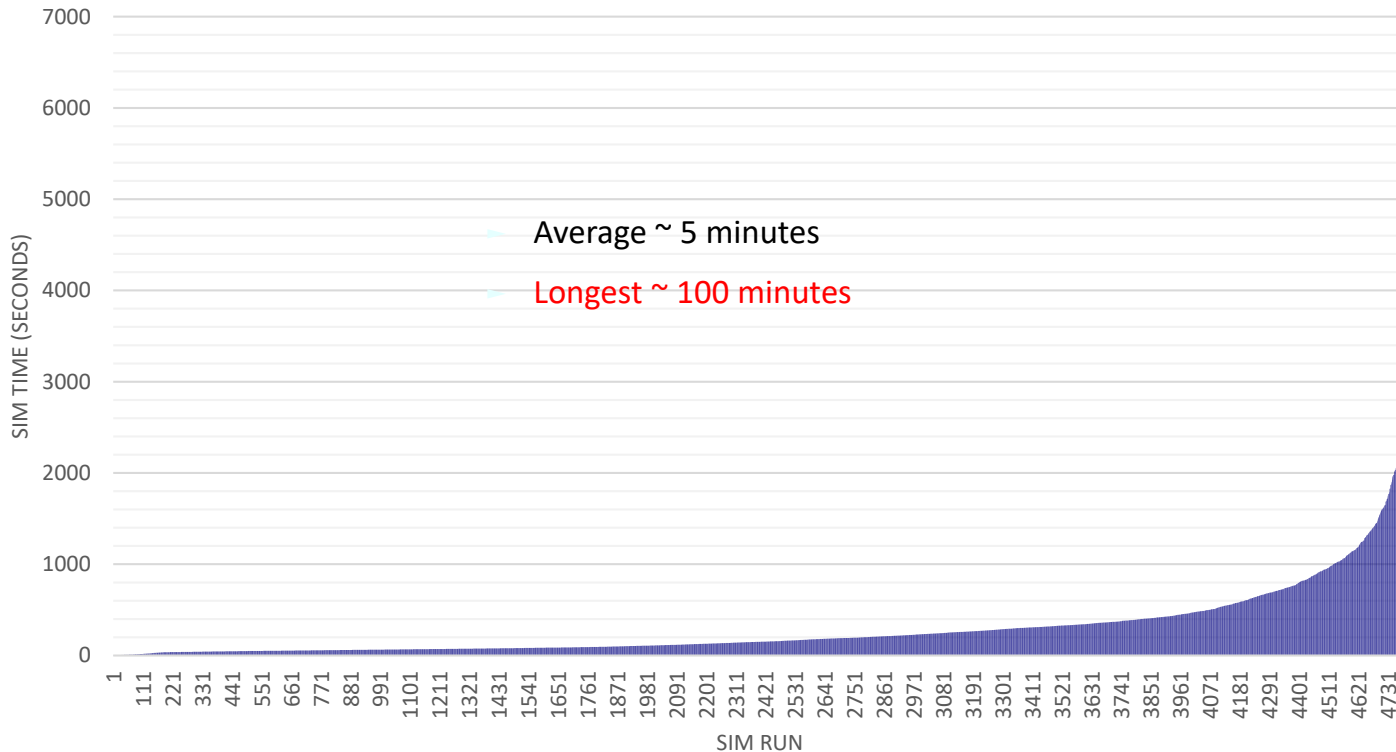

Model Validation


- Model validation relies on performance measurement:
 - No signal comparison
 - Evaluation of system metrics
- Examples:
 - BBF frequency response
 - PLL lock time and frequency error
 - Spectral analysis of mixer outputs
 - etc...

Conclusion

- **High Frequency Digital** models are achievable with reasonable degree of performance.
- Complex circuits such as **PLLs** and **mixers** can be realized in the time domain with accuracy.
- Models enable
 - **fast** test development
 - use of **randomization** at system level
 - **re-use** across disciplines
- Limitation exists but are not detrimental to **functional verification** and **coverage**

Mixer Gain

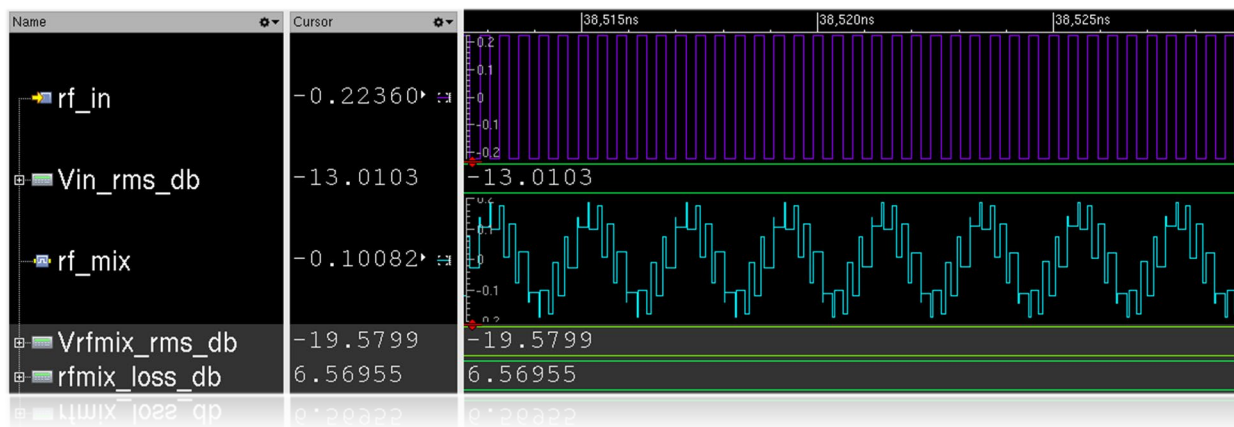- Mixer has an intrinsic gain
 - $\frac{1}{2}$ gain for filtered f_1+f_2 component
 - fundamental frequency of square wave $4/\pi$
 - filter droop at f_1-f_2 around 0.8dB
 - Some of f_1+f_2 power to remain due to 1st order attenuation
 - Expect a loss around 7dB (observer 6.56dB)



Mixer Gain

- Mixer has an intrinsic gain
 - $\frac{1}{2}$ gain for filtered f_1+f_2 component
 - Some of f_1+f_2 power to remain due to 1st order attenuation
 - Expect a loss <6dB (observed 4.5dB)

